

CSCI 210: Computer Architecture

Lecture 26: Control Path

Stephen Checkoway
Slides from Cynthia Taylor

CS History: Apple Lisa



- First mass-market PC that used a graphical user interface
- Released in 1983
- Cost \$9,995 (equivalent to \$29,400 in 2022)
- Used the Motorola 68000 CPU, the first 32-bit CPU
- Shipped with 1 MB of RAM

Control Path

- Our data path is complicated, and we don't use each element for each instruction or use it in different ways, e.g.,
 - add and addi use the ALU but not the data memory;
 - lw, sw, add, and addi require the ALU to perform an addition whereas beq and sub require the ALU to perform a subtraction
- How do we know which elements to use or what operation to have them perform? The information is encoded in the instruction itself!


What control signals do we need?

Our data path consists of four major components

 1. Instruction memory and PC register
2. Register file
3. ALU
4. Data memory


For each component, we're going to consider what control signals it needs to perform the correct operation for the instruction on the correct data

Warmup: Consider the multiplexer below. What value must the select input S_0 have for the output Z to have the same value as input B ?




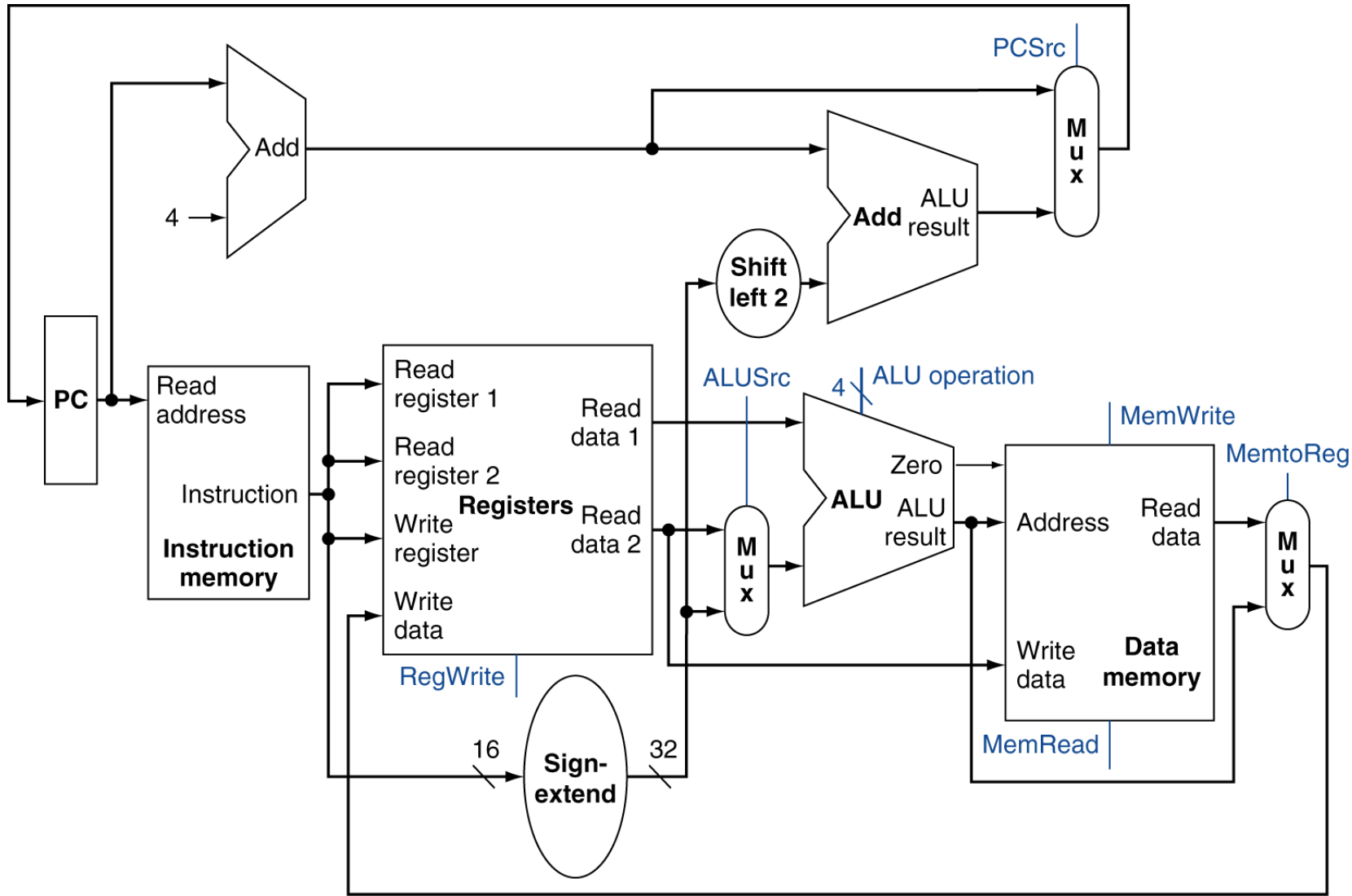- A. 0
- B. 1
- C. 2
- D. It depends on the value of A
- E. It depends on the value of both A and B

Blue inputs are some of the control signals
Today, we're going to hook some logic up to them




Recall: PLAs

 

- Derived from truth table using sum of products
- Allow us to encode arbitrary functions
- **Used to derive control signals in the data path from bits in the instruction**


Datapath With Two Control Units

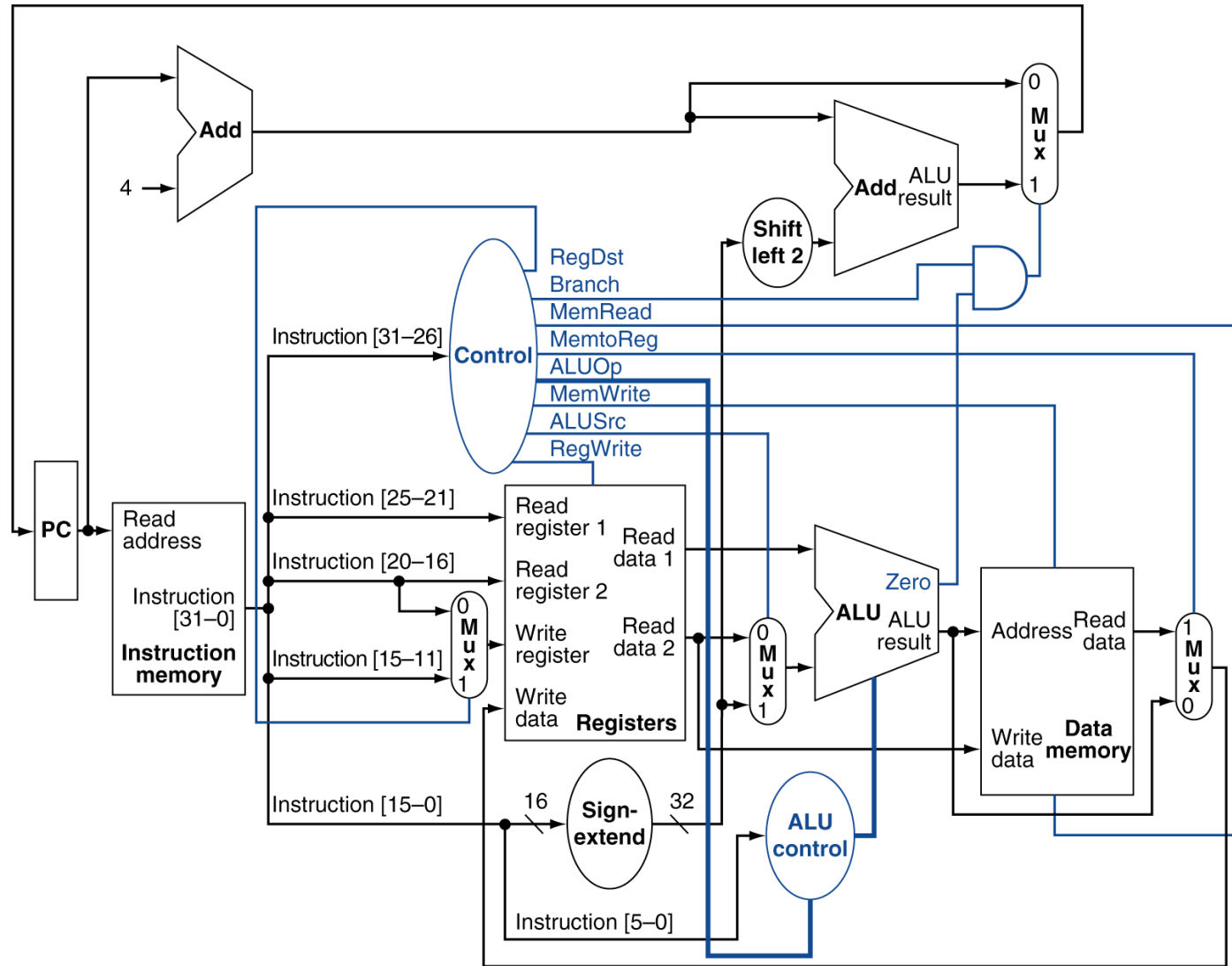

When the processor is executing the instruction

`or $t0, $t1, $t2`

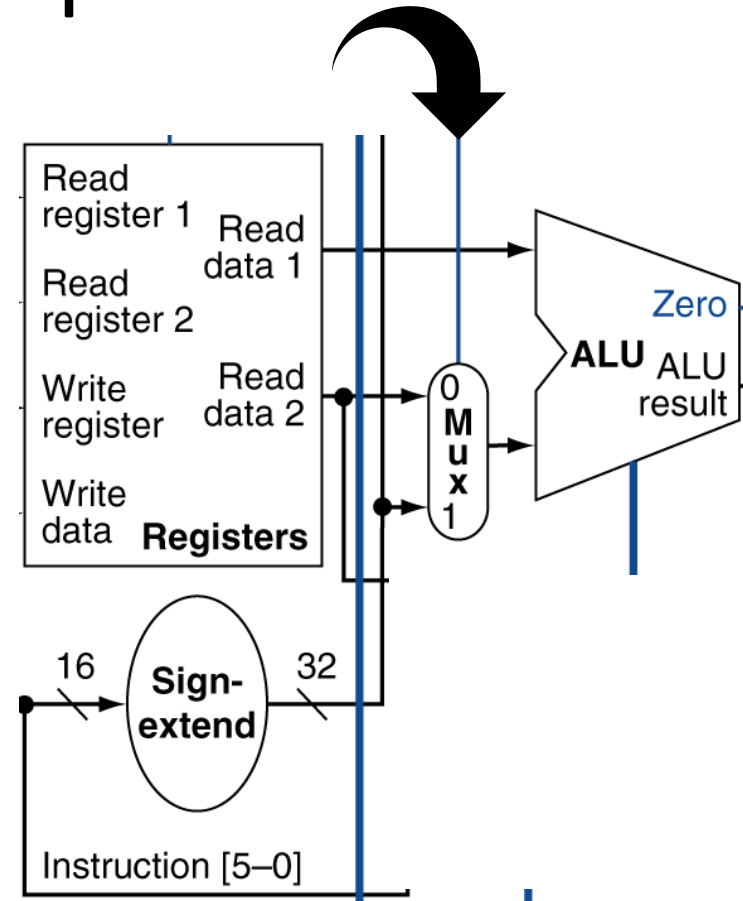what value does the select input to the multiplexer need to have?




A. 0

B. 1

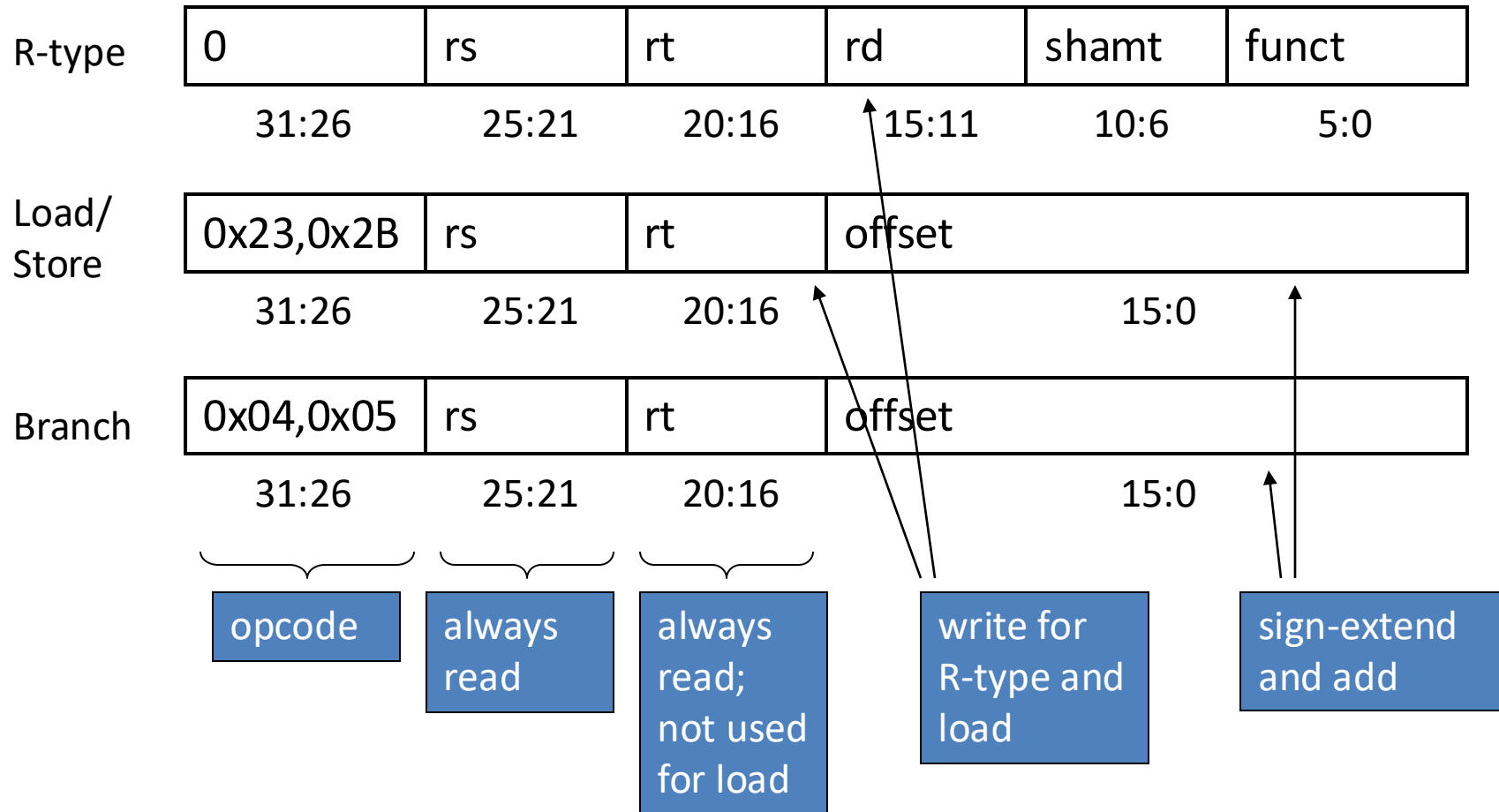C. X (a “don’t care”)

The Main Control Unit

Control signals derived from instruction opcode




Let's derive some control signals!

- We'll tackle this systematically by following the data as it flows through the data path
- Recall that every instruction has 3 steps to be executed:
 1. Fetch the instruction from instruction memory and update the PC
 2. Decode the instruction and get the operands for the ALU out of the register file or from an immediate field in the instruction
 3. Execute the instruction and store the result back into the register file



Fetching Instructions

 - Read instruction from instruction memory
- Update PC value to address of next (sequential) instruction
- PC is updated every clock cycle, so it does not need an explicit write control signal just a clock signal
- Read from memory each time, so **we don't need an explicit control signal for the instruction memory or PC**



Decoding Instructions

 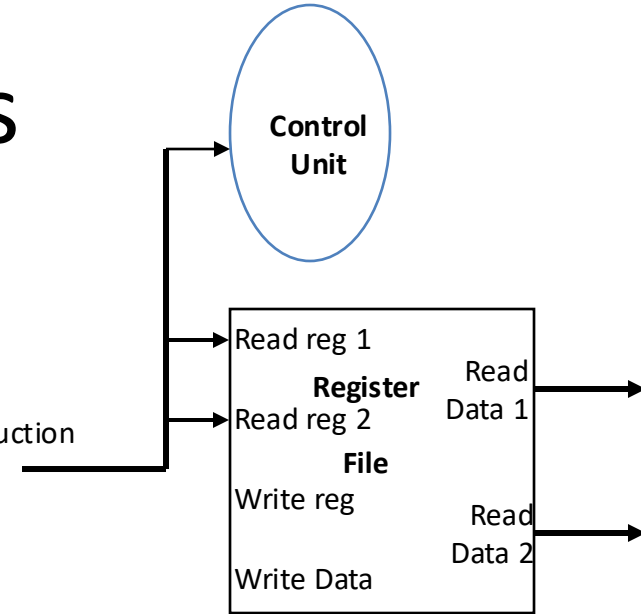- Send fetched instruction's opcode to the main control unit




- Read two values from the register file
- Register numbers are contained in the instruction (rs and rt)
- Decode happens for every instruction; this is where control signals are produced**

Producing control signals

After reading opcode

 - Produce most control signals
- Includes the ALUOp control signal—which goes to the ALU control unit—and the ALUSrc control signal which selects the ALU's second operand



When the processor is executing the instruction


`sw $s0, 28($sp)`

what value does the select input to this multiplexer need to have?

A. 0

B. 1

C. X (a “don’t care”)

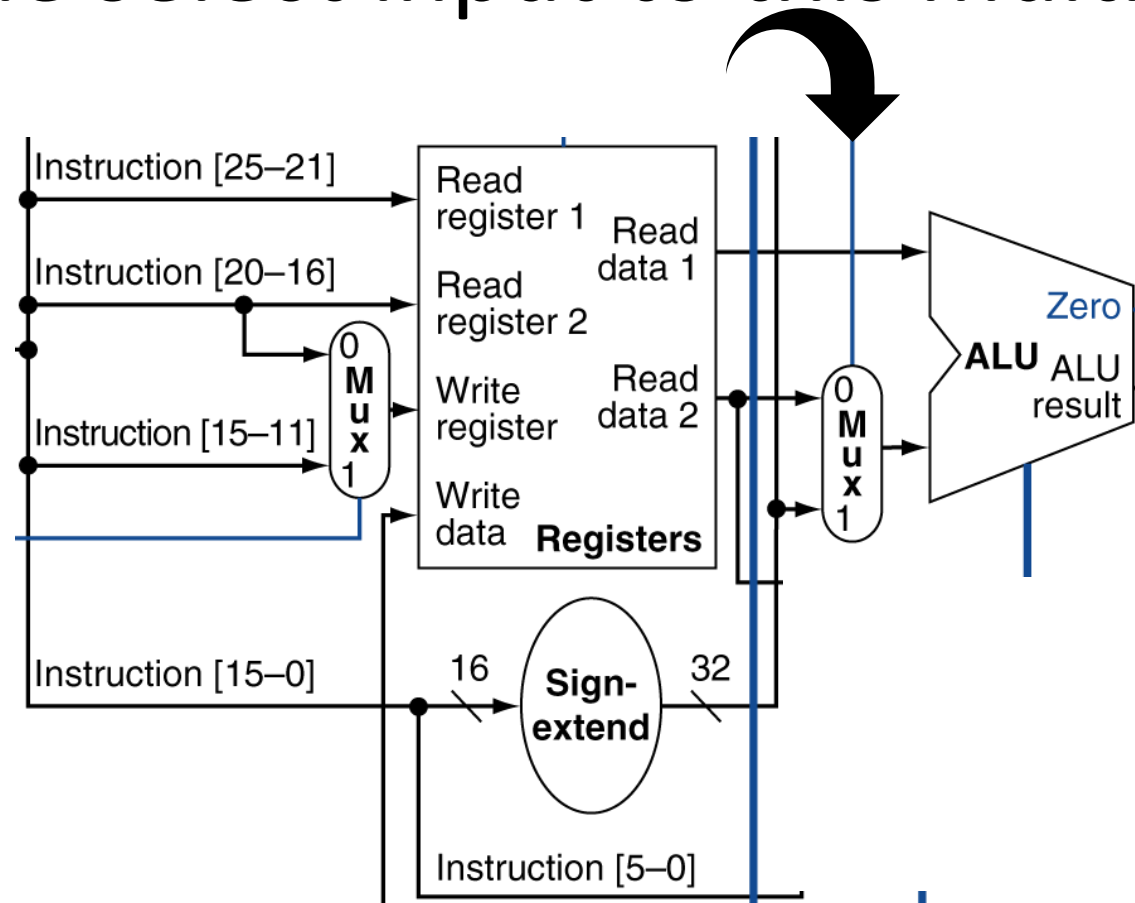

When the processor is executing the instruction


`lw $s0, 28($sp)`

what value does the select input to this multiplexer need to have?

A. 0

B. 1

C. X (a “don’t care”)

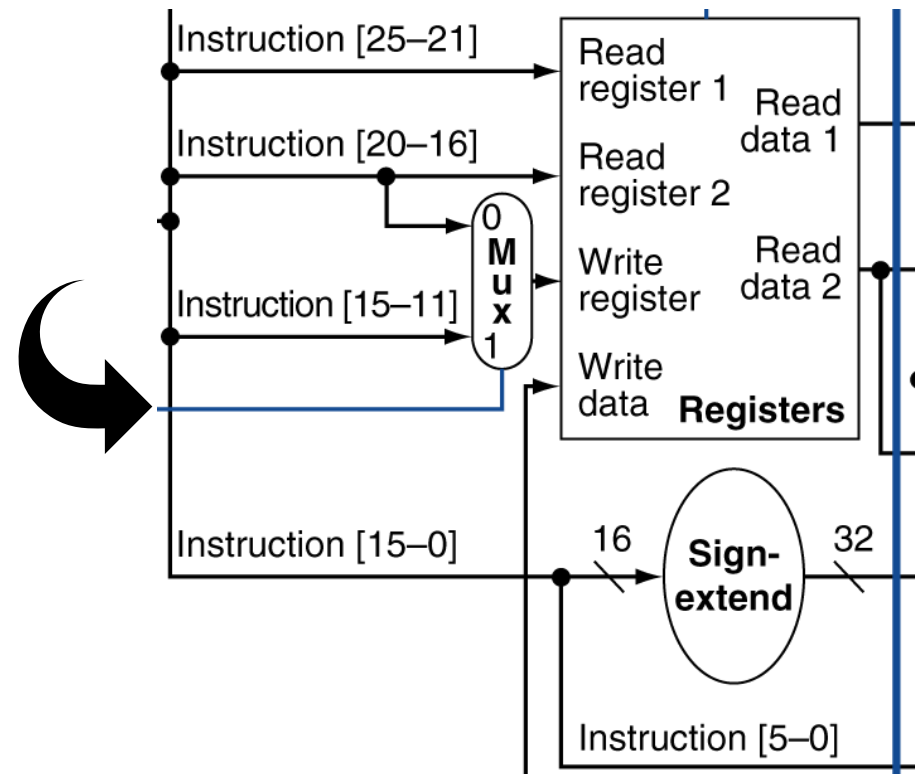

Opcode	rs	rt	address
--------	----	----	---------

31:26


25:21

20:16

15:0

For load/store, our ALU operation will be

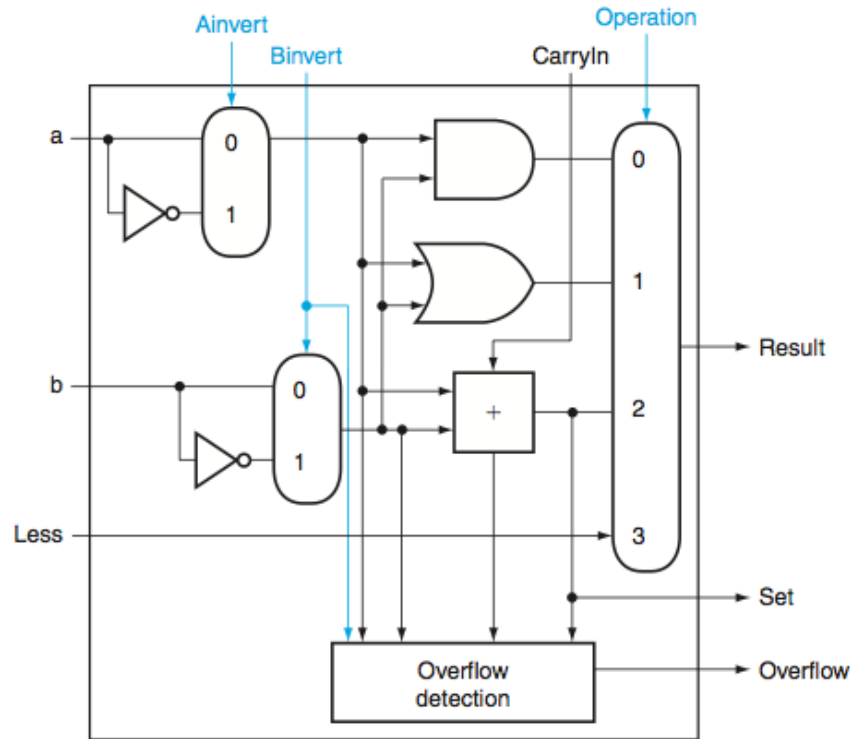- A. Add
- B. And
- C. Set less than
- D. Subtract
- E. None of the above





lw \$t0, 4(\$t1)

ALU Control Unit


- Combinational logic (the main control unit) derives 2-bit ALUOp signal from opcode
- ALU Control Unit takes ALUOp and instruction funct field as inputs and derives a 4-bit ALU control signal

opcode	ALUOp	Operation	ALU function
lw	00	load word	add
sw	00	store word	add
beq	01	branch equal	subtract
R-type	10	arithmetic/logic	depends on funct

  

ALU Control signal

 
- ALU used for
 - Load/Store: op = add
 - Branch: op = subtract
 - R-type: op depends on funct field



ALU control	Function	Ainvert	Binvert/CarryIn0	Operation
0000	AND	0	0	00
0001	OR	0	0	01
0010	add	0	0	10
0110	subtract	0	1	10
0111	set-on-less-than	0	1	11
1100	NOR	1	1	00

ALU Control

 
Takes as input 2-bit ALUOp (derived from opcode) and 6-bit funct field; outputs 4 bits




Instruction	ALUOp	funct	ALU function	Ainvert	Binvert	ALU operation
load word	00 (add)	XXXXXX	add	0	0	10 (add)
store word	00 (add)	XXXXXX	add	0	0	10 (add)
branch equal	01 (subtract)	XXXXXX	subtract	0	1	10 (add)
add	10 (r-type)	100000	add	0	0	10 (add)
subtract		100010	subtract	0	1	10 (add)
AND		100100	AND	0	0	00 (and)
OR		100101	OR	0	0	01 (or)
NOR		100111	NOR	1	1	00 (and)
set-on-less-than		101010	set-on-less-than	0	1	11 (less)

Executing R Format Operations

 - R format operations (**add**, **sub**, **slt**, **and**, **or**)



 
- perform operation (specified by **funct**) on values in **rs** and **rt**
- store the result back into the Register File (into location **rd**)



Note that Register File is not written every cycle (e.g., **sw**), so we need an explicit write control signal for the Register File

instruction control signals for ADD?


Select	RegDst	MemToReg
A	0	X
B	1	X
C	0	1
D	1	0
E	None of the above	

 

R-type	0	rs	rt	rd	shamt	funct
	31:26	25:21	20:16	15:11	10:6	5:0

R-Type Instruction

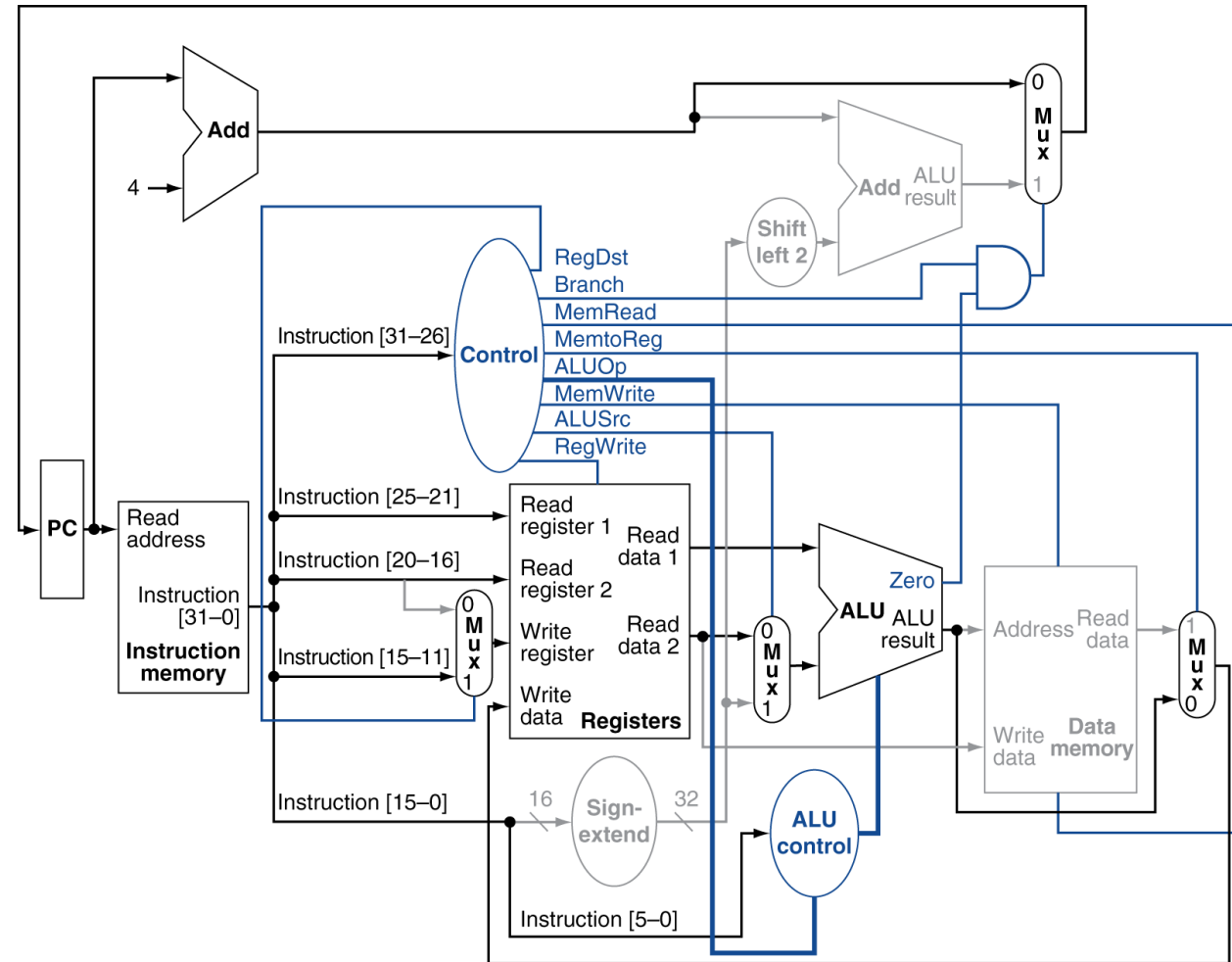ALUOp = 00 (add)
 ALUOp = 01 (subtract)
 ALUOp = 10 (R-type)




RegDst	
Branch	
MemRead	
MemtoReg	
ALUOp	
MemWrite	
ALUSrc	
RegWrite	


R-type	0	rs	rt	rd	shamt	funct
	31:26	25:21	20:16	15:11	10:6	5:0

Executing Load and Store Operations

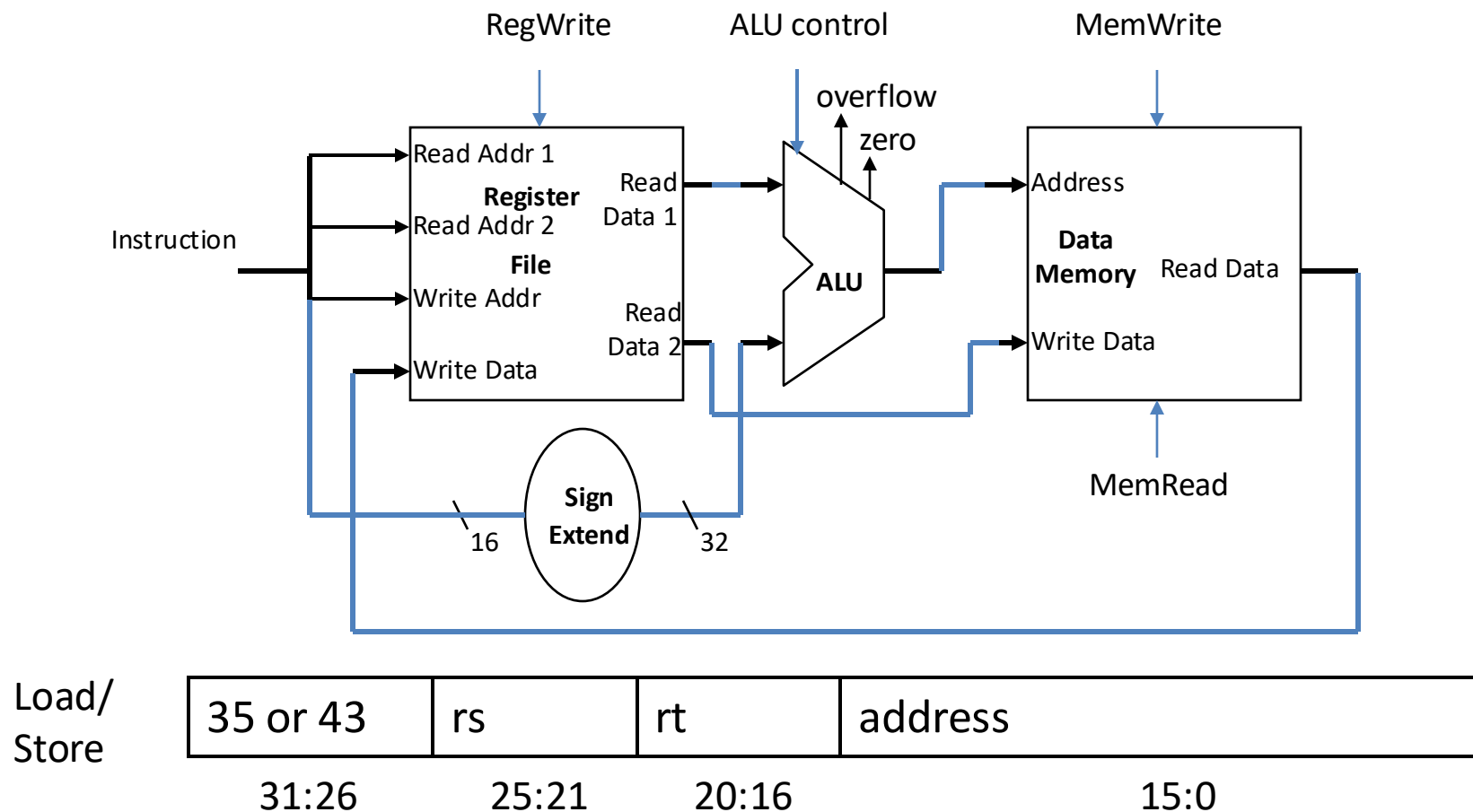- compute memory address by adding base register to 16-bit signed-extended offset field
- **store** value written to the Data Memory
- **load** value read from the Data Memory, written to the Register File



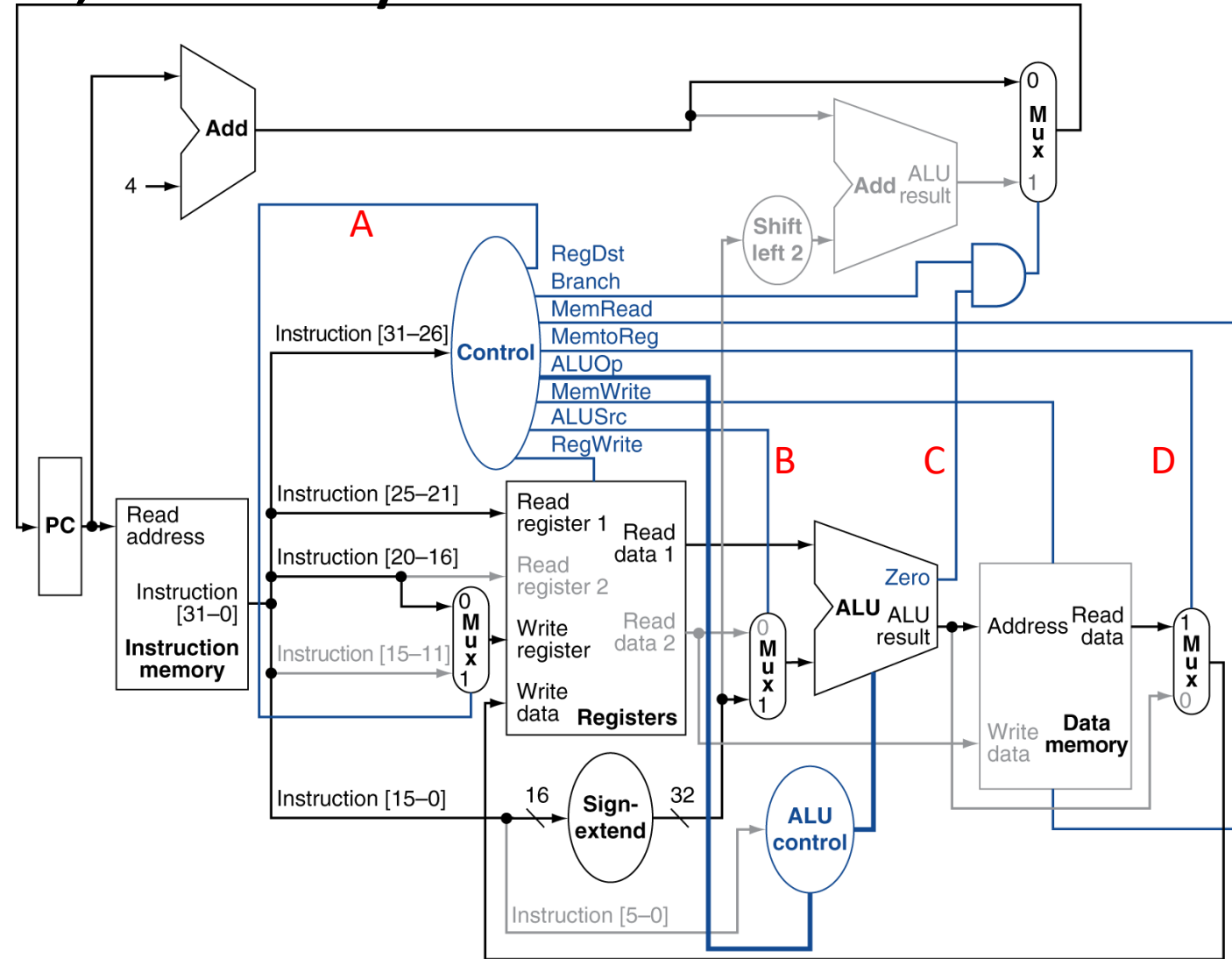Which wire, if always set to 1 would break lw?




Load/
Store

35 or 43	rs	rt	address
31:26	25:21	20:16	15:0

Load Instruction

 ALUOp = 00 (add)
ALUOp = 01 (subtract)
ALUOp = 10 (R-type)




RegDst	
Branch	
MemRead	
MemtoReg	
ALUOp	
MemWrite	
ALUSrc	
RegWrite	

Load/
Store

35 or 43	rs	rt	address
31:26	25:21	20:16	15:0

Executing Branch Operations


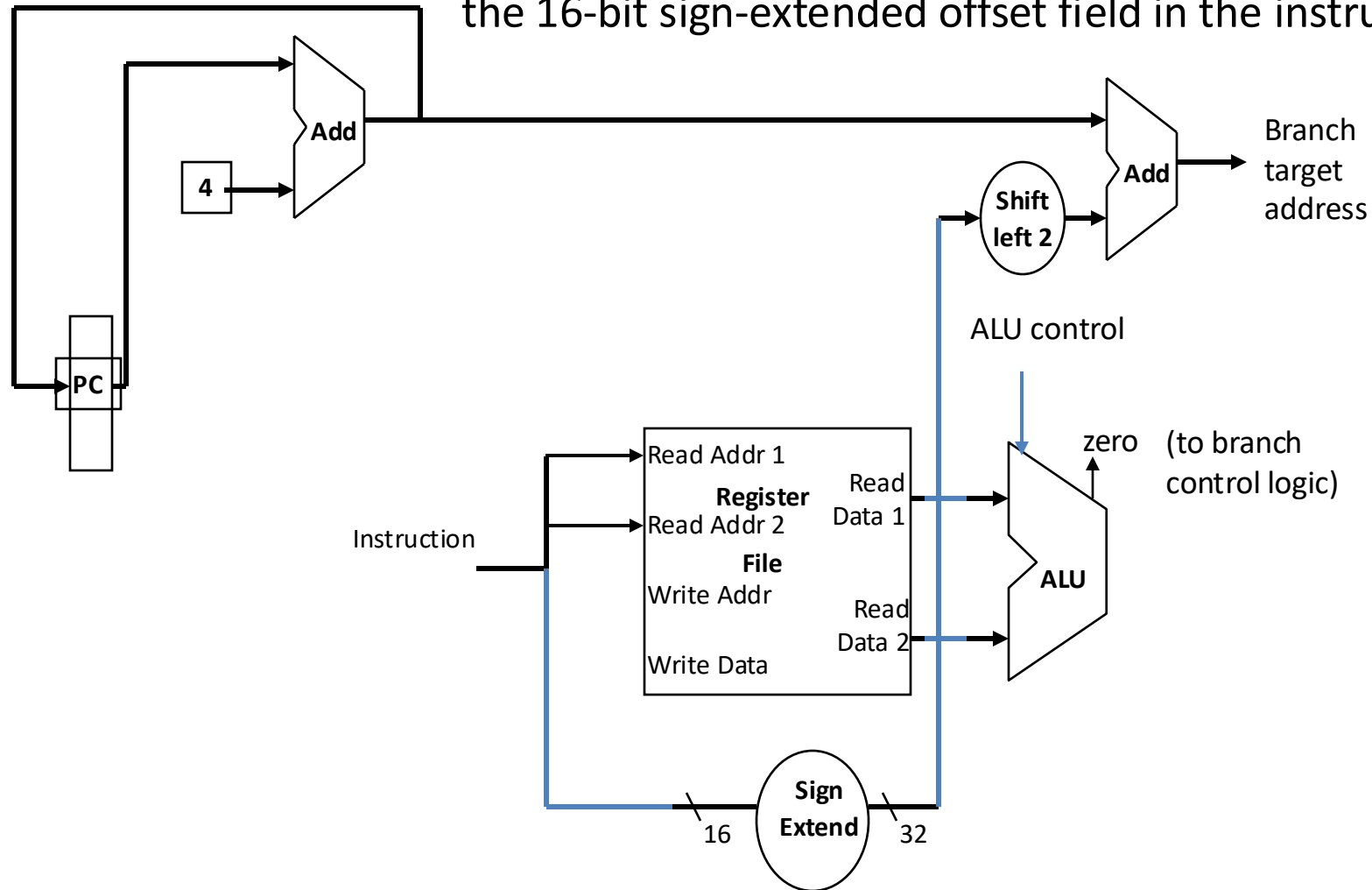
- Branch operations involve
 - compare the operands read from the Register File during decode for equality (**zero** ALU output)
 - compute the branch target address by adding the updated PC to the 16-bit sign-extended offset field in the instruction



Branch-on-Equal Instruction

ALUOp = 00 (add)
 ALUOp = 01 (subtract)
 ALUOp = 10 (R-type)

RegDst	
Branch	
MemRead	
MemtoReg	
ALUOp	
MemWrite	
ALUSrc	
RegWrite	

 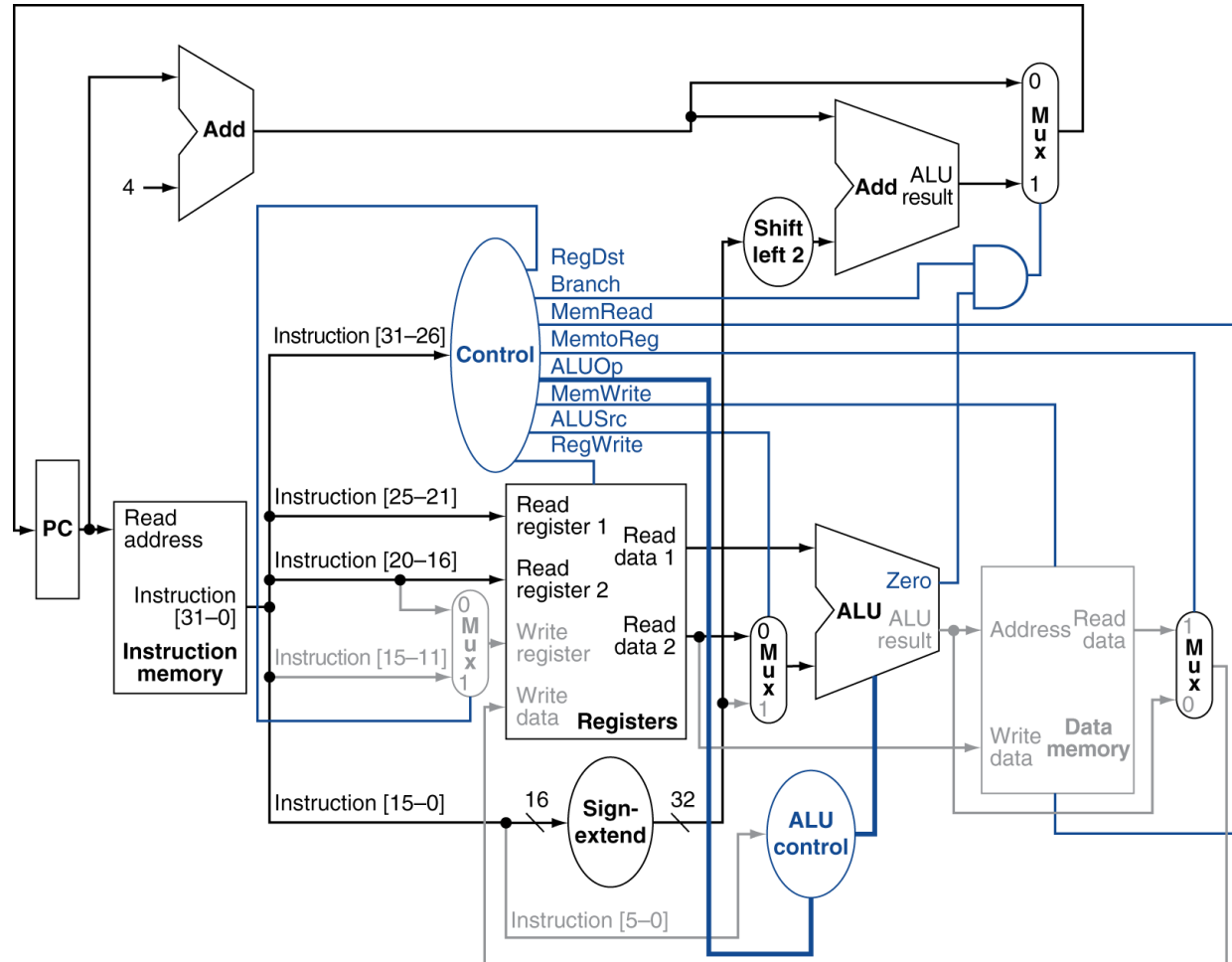

Control Truth Table


		R-format	lw	sw	beq
Opcode		000000	100011	101011	000100
Outputs	RegDst	1	0	x	x
	ALUSrc	0	1	1	0
	MemtoReg	0	1	x	x
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

ALUOp = 00 (add)

ALUOp = 01 (subtract)


ALUOp = 10 (R-type, use funct to determine ALUCtrl signals)

Implementing Jumps

 


- Jump uses word address
- Update PC with concatenation of
 - Top 4 bits of PC + 4
 - 26-bit jump address
 - 00

Datapath With Jumps Added

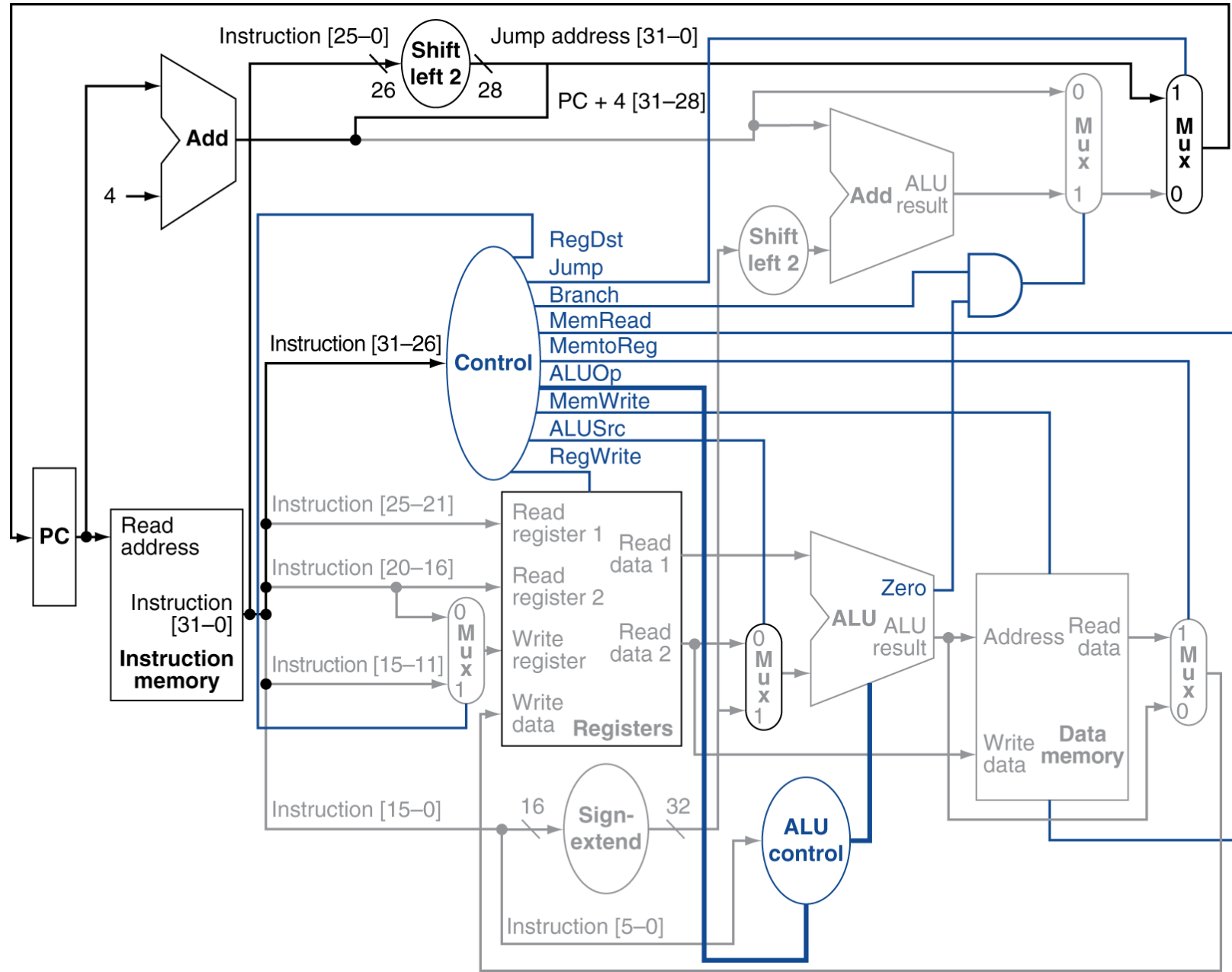

What will the Signals for Jump be?

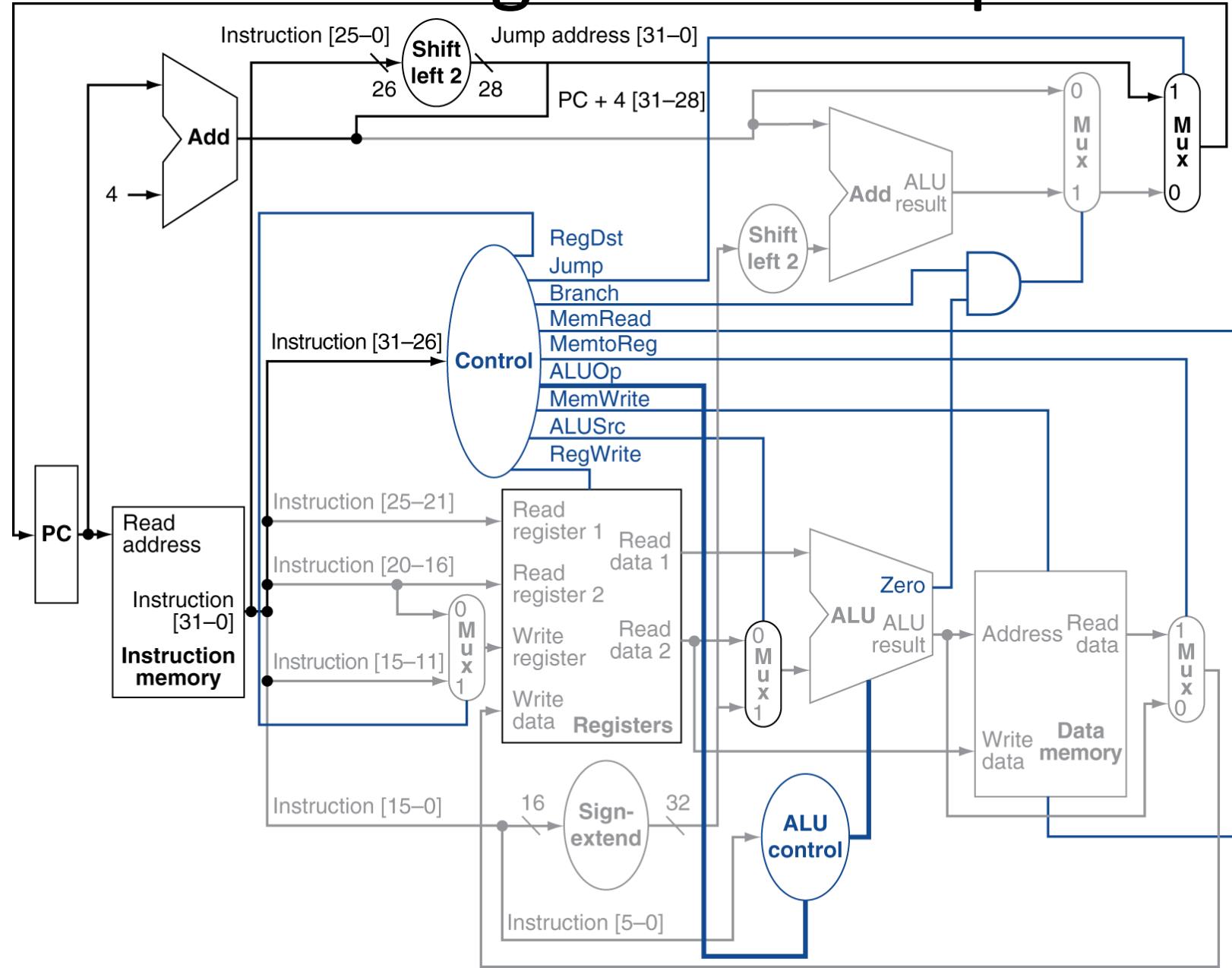ALUOp = 00 (add)
 ALUOp = 01 (subtract)
 ALUOp = 10 (R-type)



RegDst	
Jump	
Branch	
MemRead	
MemtoReg	
ALUOp	
MemWrite	
ALUSrc	
RegWrite	

RegDst	
Jump	
Branch	
MemRead	
MemtoReg	
ALUOp	
MemWrite	
ALUSrc	
RegWrite	

