

CSCI 210: Computer Architecture

Lecture 17: Arithmetic Logic Unit

Stephen Checkoway
Slides from Cynthia Taylor

CS History: Mohamed M. Atalla



أحمد بن طارق, CC BY-SA 4.0

- Born in 1924 in Egypt
- Invented the MOSFET (metal-oxide semiconductor field-effect transistor) with Dawon Kahng in 1960
- First truly compact transistor
- MOS transistors are the fundamental building blocks of today's electronics
- Most manufactured device in history
 - 13 sextillion MOS transistors manufactured as of 2018
- Went on to start a cybersecurity company, invented the “Atalla box” which secured most ATMs in the past


Arithmetic and Logical Unit (ALU)

- Need to use digital logic to build a unit that can do basic computation – math, logical operations, etc.
- Needs to be 32 bits wide, since MIPS has 32 bit words.
 - Build out of 1-bit ALUs

Our ALU will support the following operations:


- Add
- Sub
- And
- Or
- Nor
- Nand
- Set less than

1-bit ALU: AND and OR

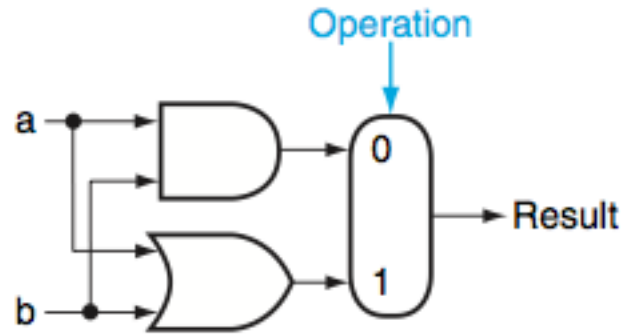

- Inputs go to both AND and OR
- Multiplexer selects AND or OR function for output

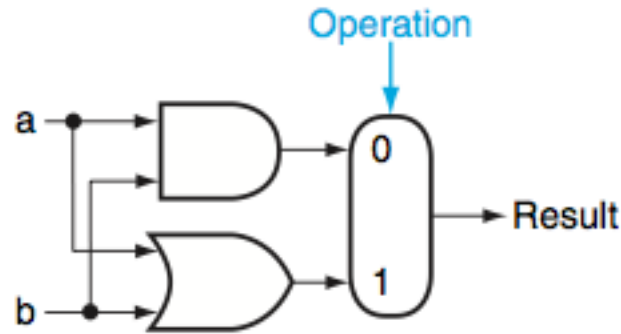If $a = 0$, $b = 1$, and operation = 1, what is Result?



- A. 0
- B. 1
- C. Impossible to say without additional information

1-bit Binary Addition

$$0 + 0 = 0$$

$$0 + 1 = 1$$


$$1 + 0 = 1$$

$$1 + 1 = 10$$

Need to account for two output bits!

Half Adder

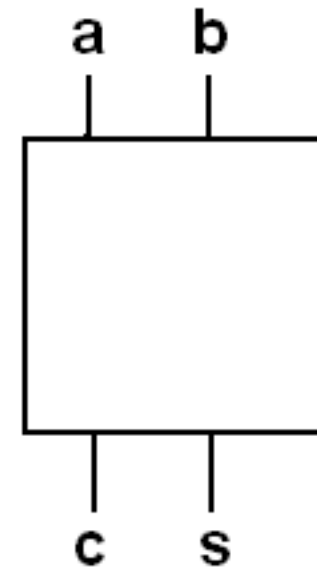- Inputs a, b
- Outputs sum and carry out
- Sum is the 1-bit result of adding a and b
- Carry out is the carry in the normal sense



Below is the truth table for the SUM output of a half adder.
What is the Boolean algebra function that will give us this truth table?

a	b	Sum
0	0	0
0	1	1
1	0	1
1	1	0

A. $a \text{ OR } b$

D. $a \text{ NOR } b$

B. $a \text{ XOR } b$

E. None of the above

C. $a \text{ AND } b$

Below is the truth table for the CARRY output of a half adder.
What is the Boolean algebra function that will give us this truth table?

a	b	Carry out
0	0	0
0	1	0
1	0	0
1	1	1

A. $a \text{ OR } b$

D. $a \text{ NOR } b$

B. $a \text{ XOR } b$

E. None of the above

C. $a \text{ AND } b$

Binary Addition with Arbitrary Number of Bits


- Just like regular, grade school addition
 - Make sure we carry a 1 to the next digit when needed
- Now we need to be able to account for the carry-in from the next least-significant bit
- Example: $7+5$

Addition

- We're going to chain together thirty-two 1-bit "full adders"
- Each full adder has
 - 3 inputs: a, b, and carry in (which is the carry out of the previous bit)
 - 2 outputs: sum and carry out

```
  1 1 1
0111
0101
———
1100
```


Full Adder from Half Adders

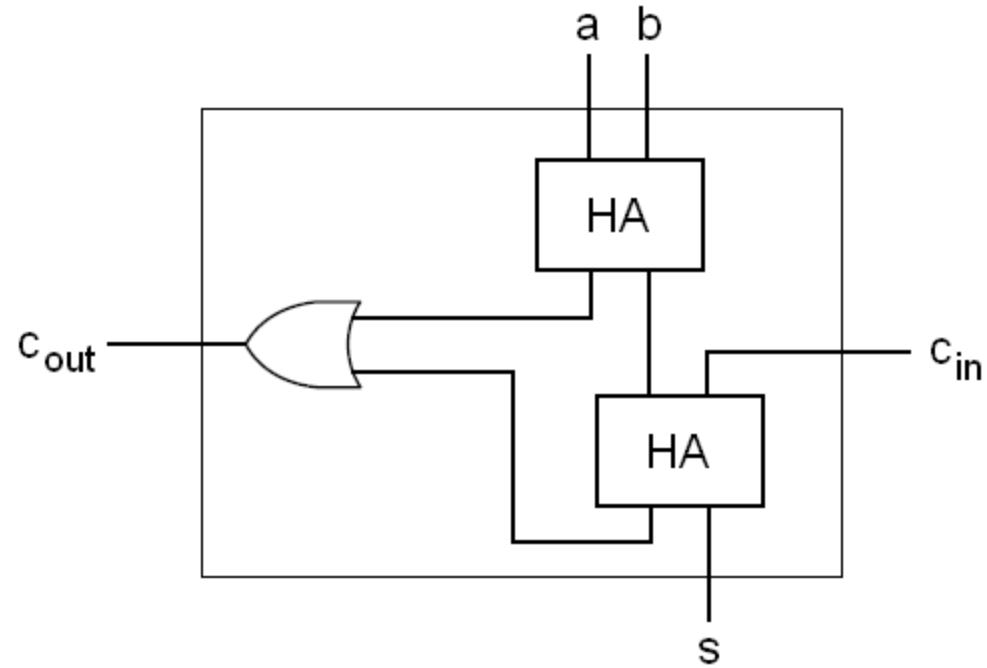


Build a full adder from two half adders

What if both half adders have carry-out?

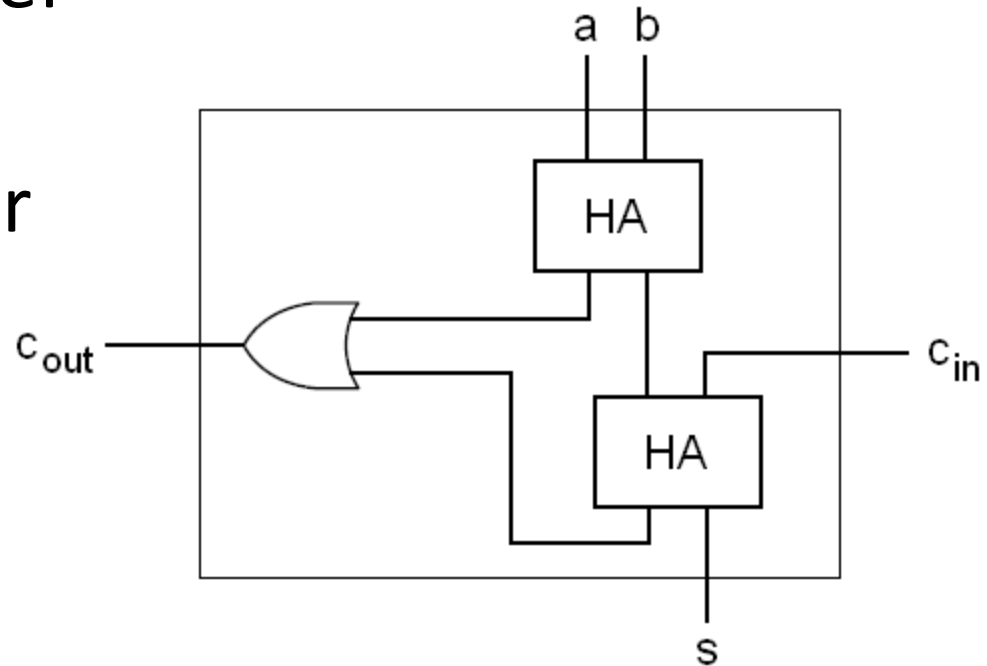- A. We will get the wrong answer
- B. We will ignore it; the answer will still be correct
- C. That will never happen
- D. None of the above




Ripple-Carry Adder

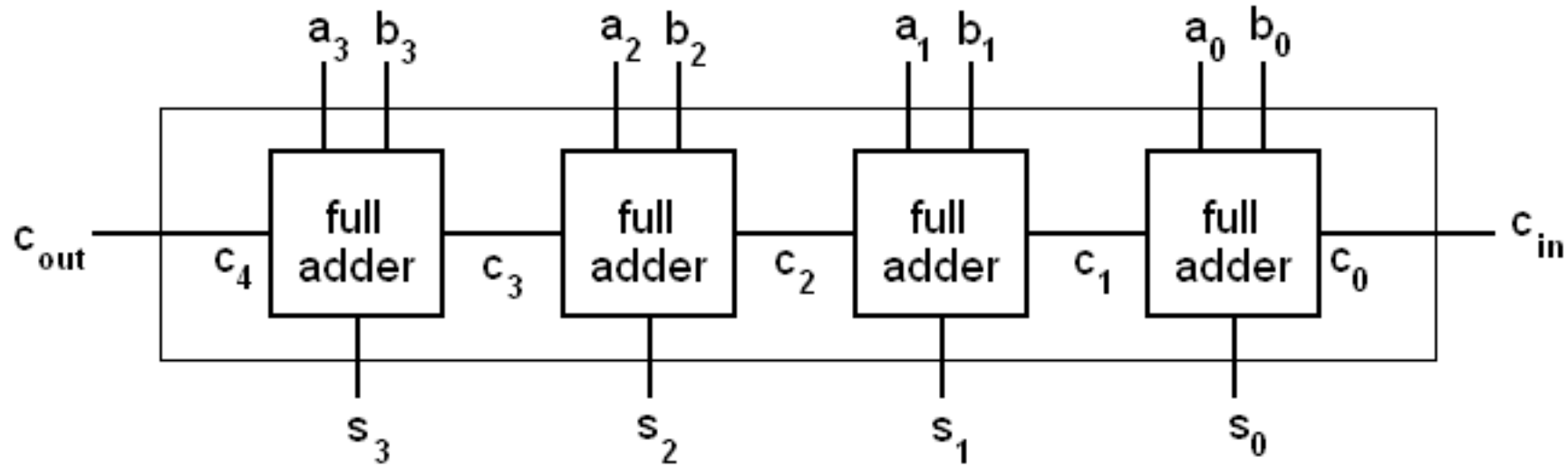

- Create adder for an arbitrary number of bits simply by connecting carry-out from adder $n-1$ to the carry-in for adder n
- Carry bit “ripples” up

1-bit ALU

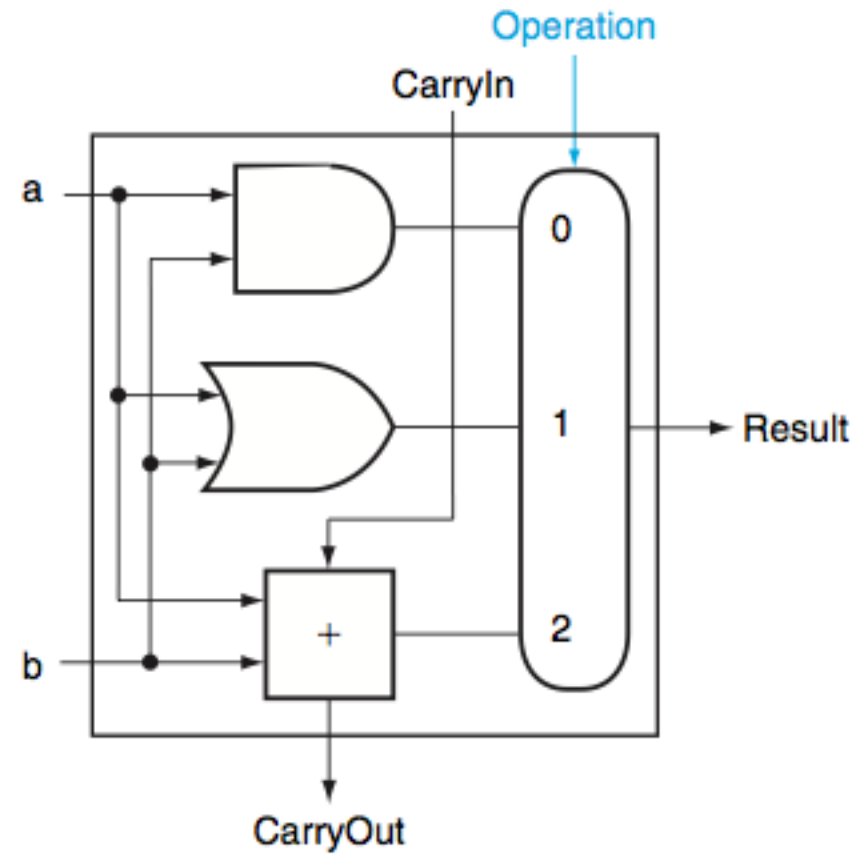


Subtraction: $a - b$

- Just add negative version of b !
- To negate operand, take its two's complement
 - Invert each bit
 - Add one


We can use a NOT gate to invert the input. To add one to the input, we should

- A. Set the carry-in for the least significant bit to 1
- B. Add a new “subtract” input to each full adder that we set to 1 for subtraction and 0 for addition

C. Do something else

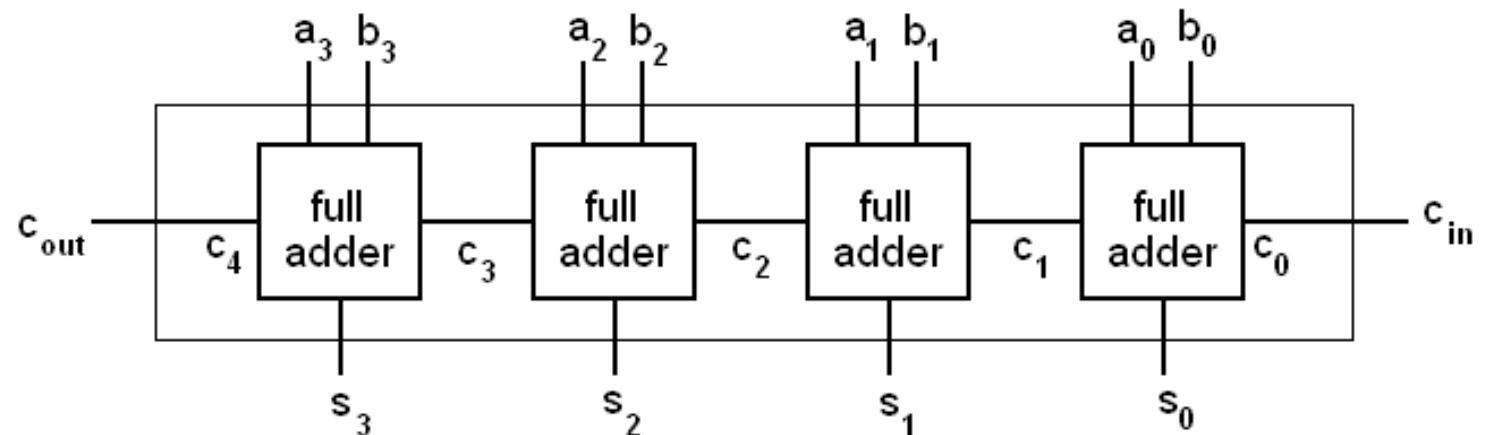


1-bit ALU with Subtraction

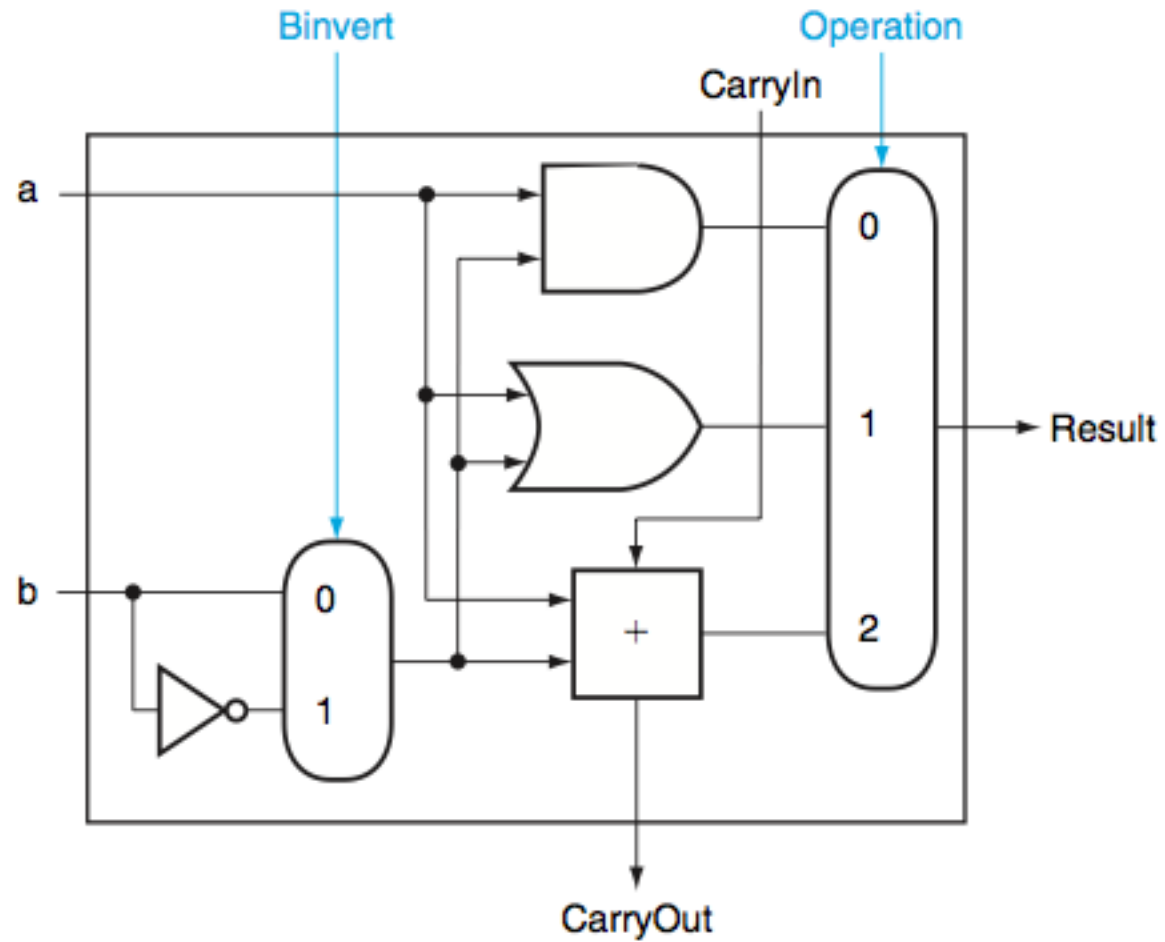

This 1-bit ALU supports 4 operations (and, or, add, sub). How many bits are required in the operation input signal, and *why* do we need that many?

- A. 1
- B. 2
- C. 3
- D. 4

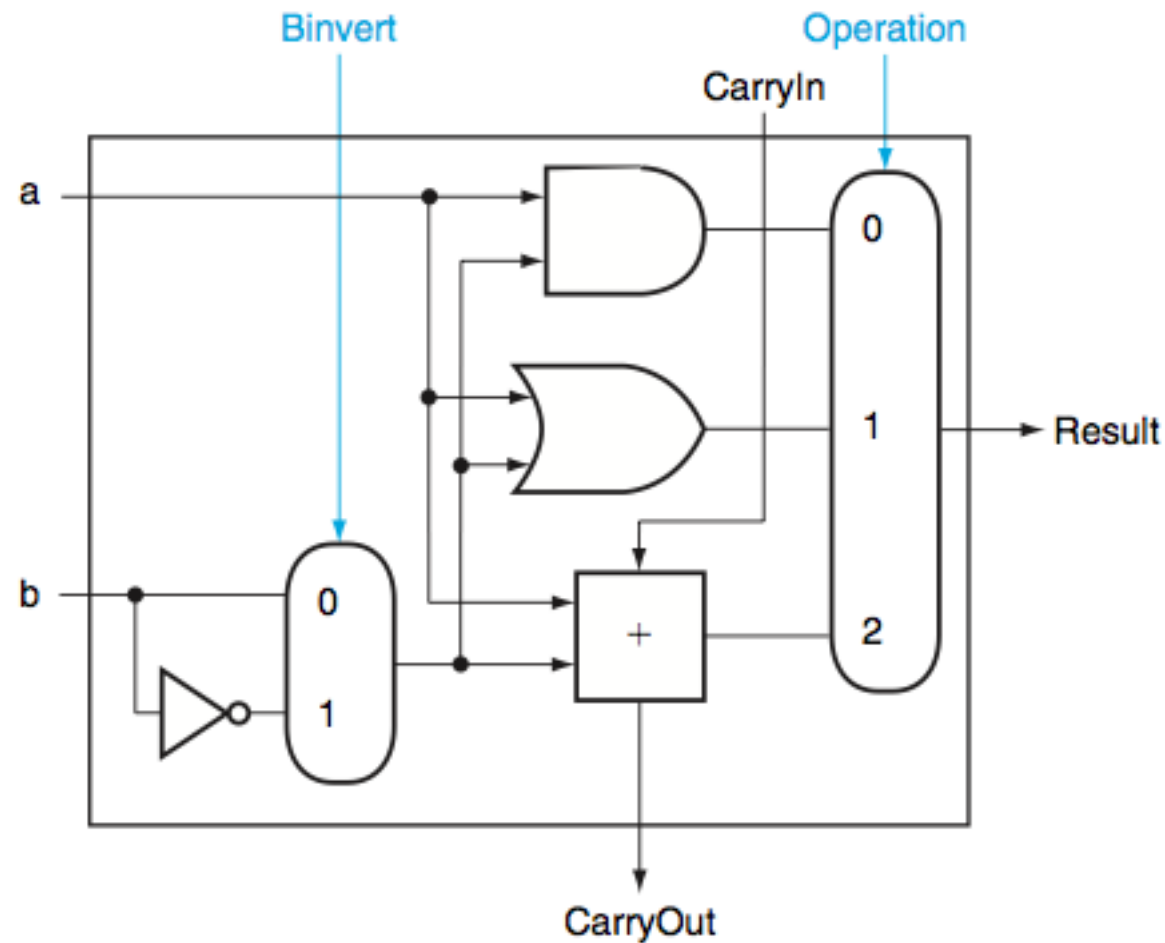


Adding NOR

- Want to add NOR functionality
- DeMorgan's Law
 - $\overline{(A+B)} = \bar{A} \bar{B}$


To add NOR to the ALU, we need to add

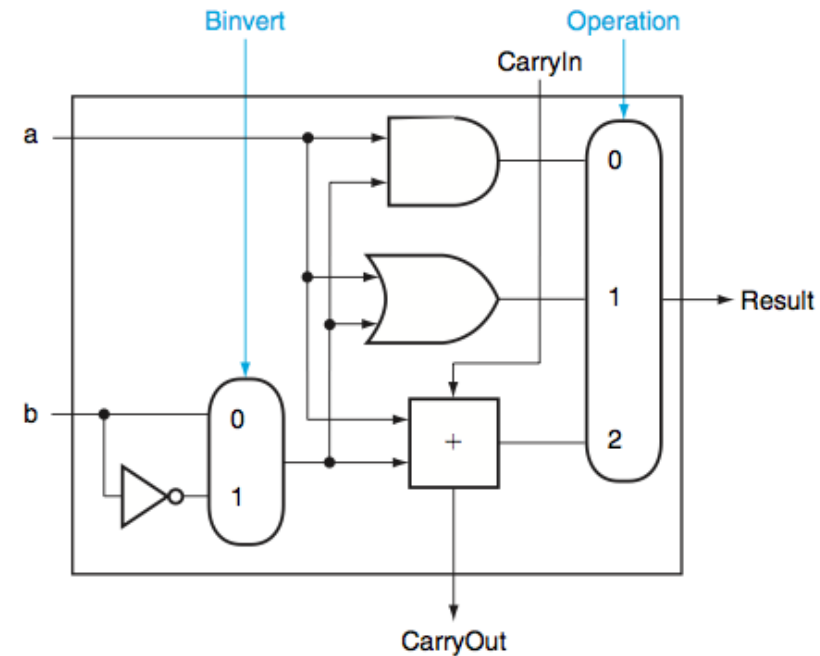- A. Nothing
- B. The ability to invert A
- C. A NOR gate
- D. Something else



DeMorgan's Law
$$\overline{(A+B)} = \bar{A} \bar{B}$$


1-bit ALU with NOR

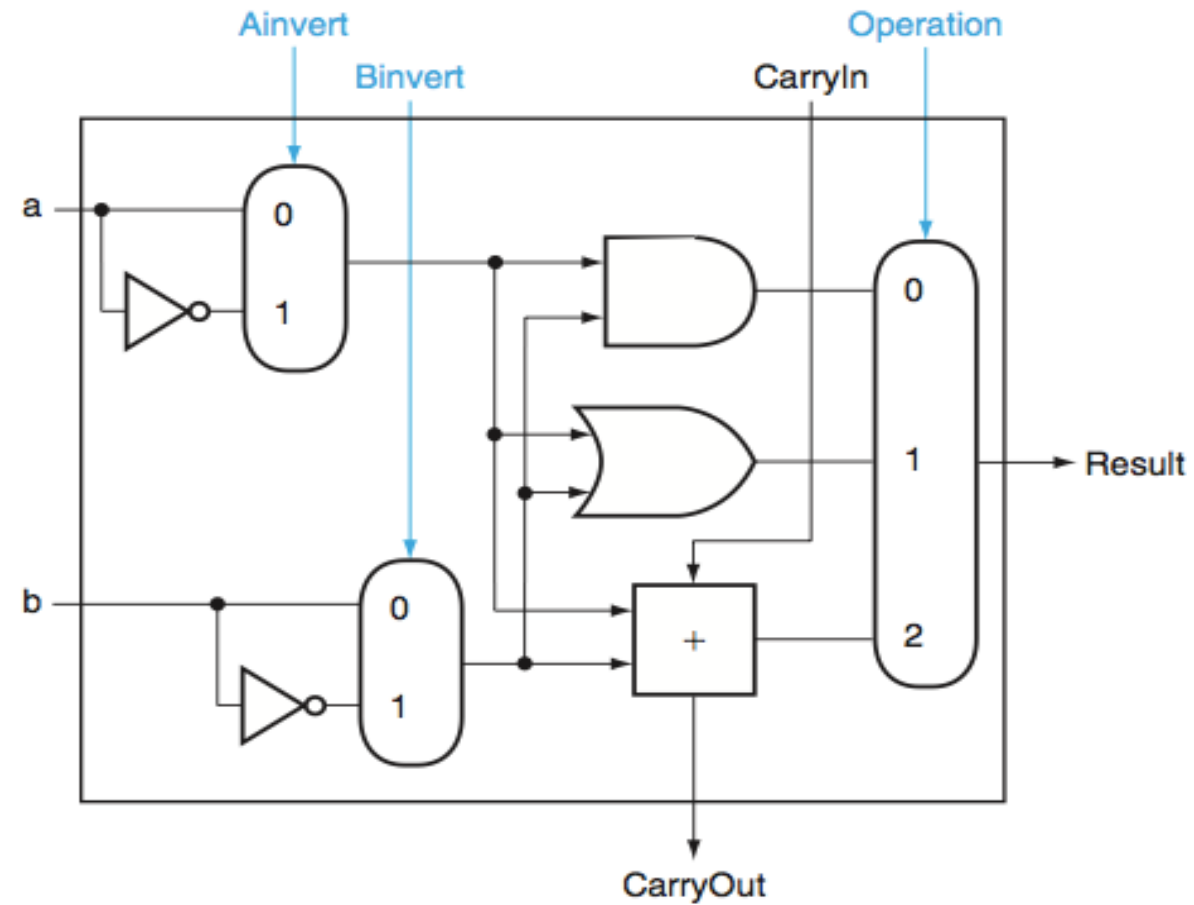

Adding slt

- `slt rd, rs, rt`
 - `rd = 1` if `rs < rt`, and `0` otherwise
- Only sets least significant bit
 - All other bits are `0`

1-bit ALU: Add new input for slt

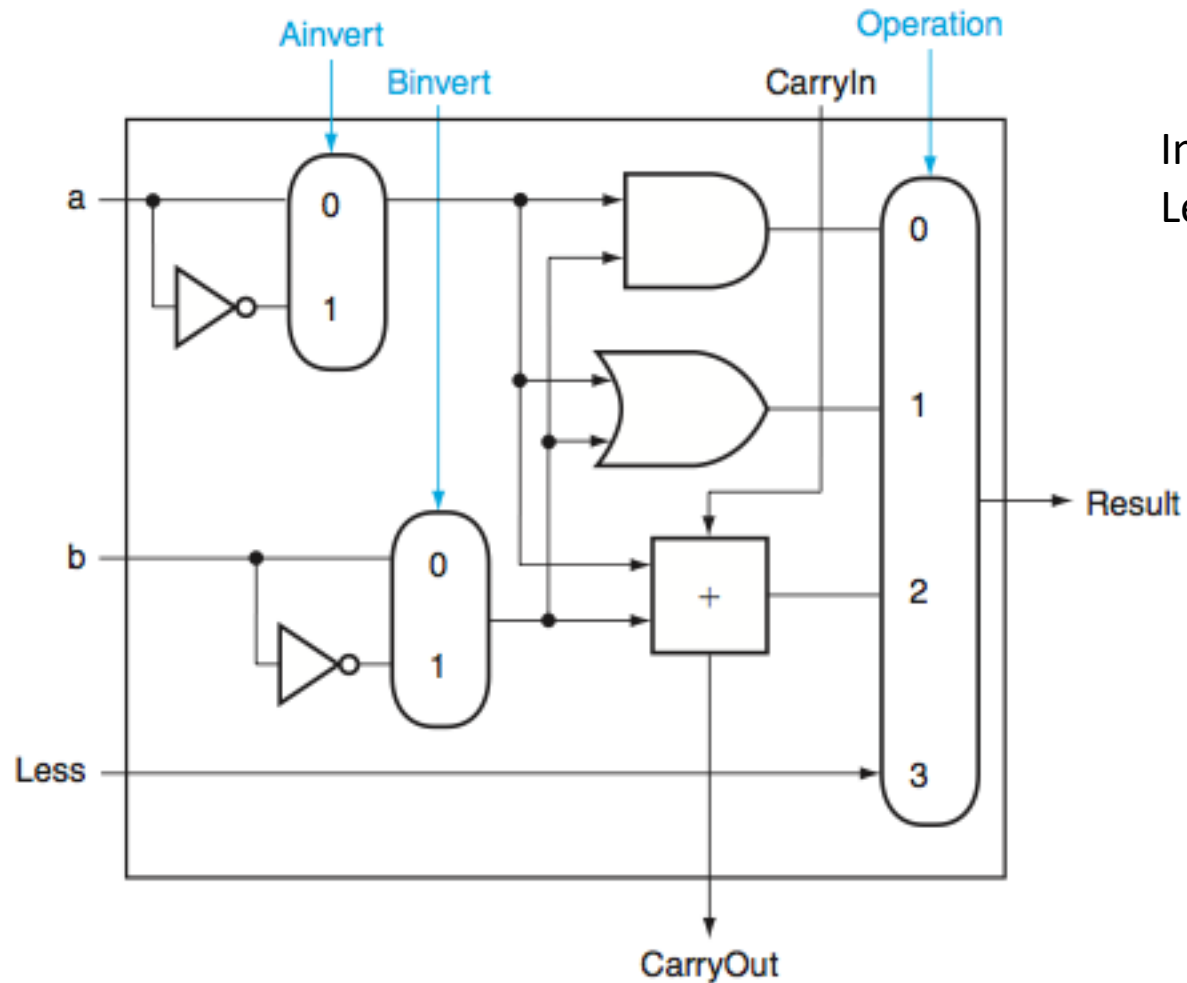


In all but the least significant bit,
Less will always be 0


How do we tell if $a < b$?

- Subtract b from a
- If $a - b < 0$, then $a < b$
- We can check this by checking the most significant bit
 - $\text{MSB} = 1$, $a < b$

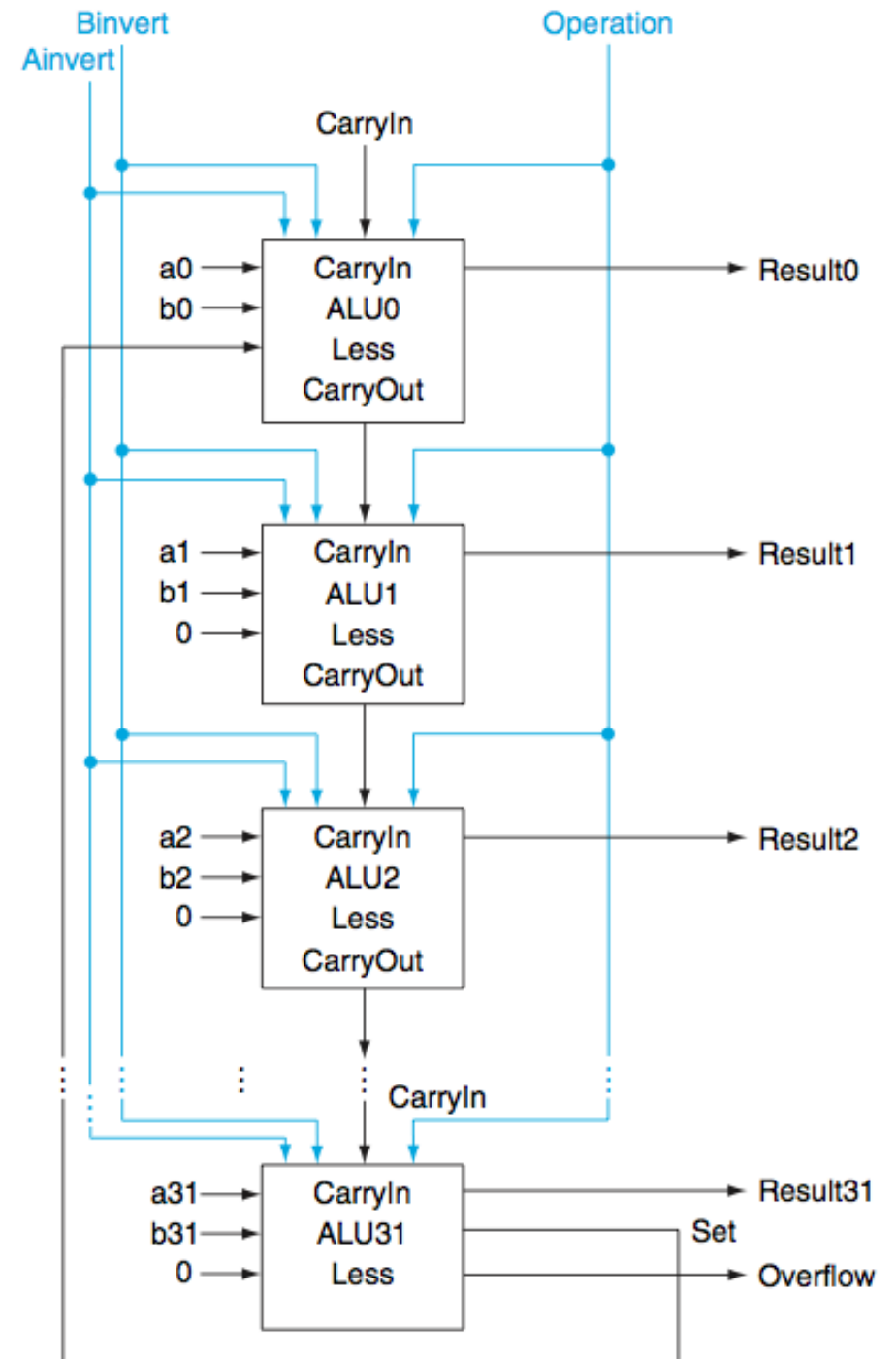- Problem: Output is at most significant bit, we need it at least significant bit
- Solution: Special ALU for Most Significant Bit, with output for SLT
- Connect Set output to Less input for least significant bit



1-bit ALU for the Most Significant Bit

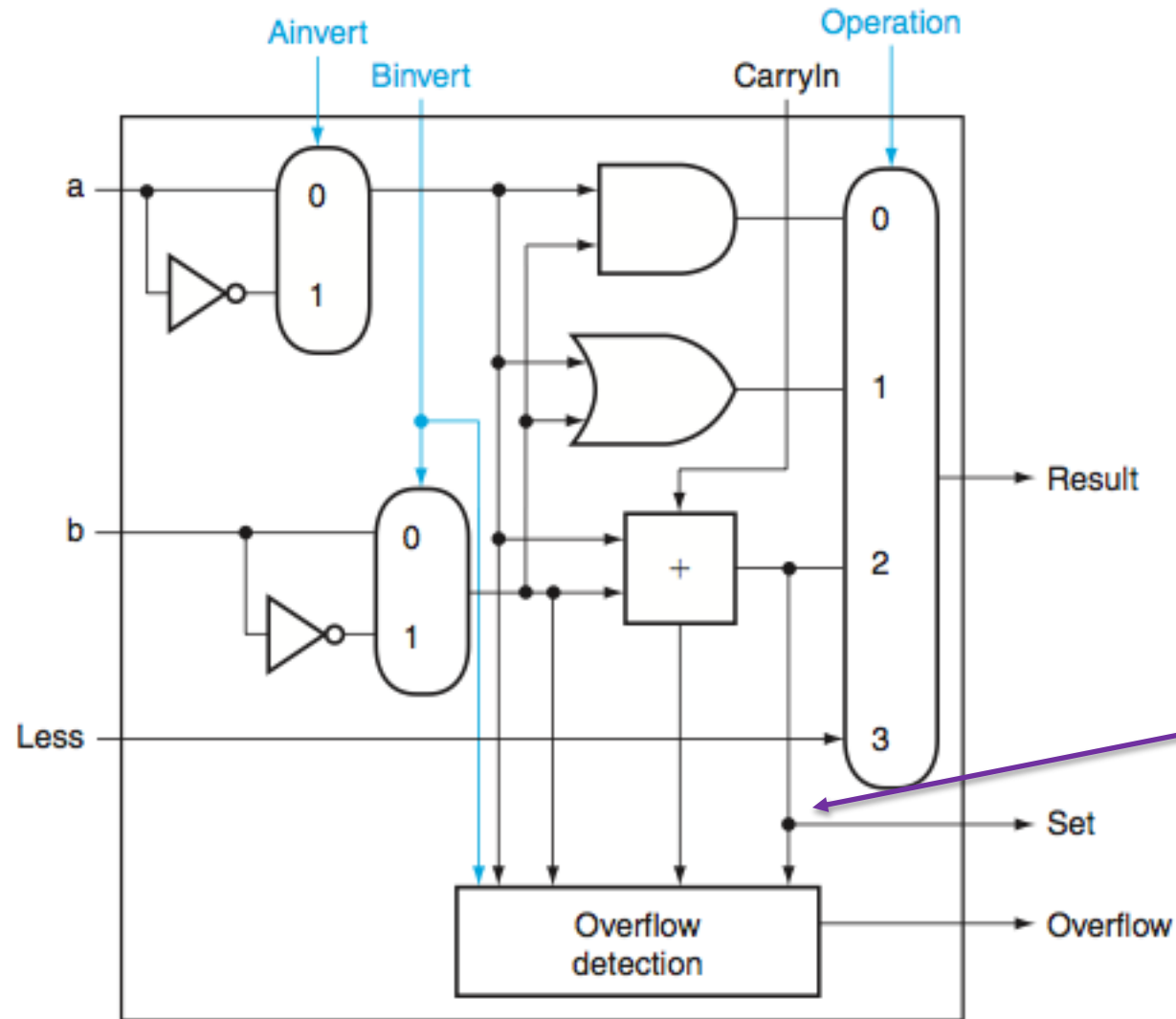

This doesn't
always work!
You'll fix it in
problem set 6

Recall: Overflow

- If we add two n -bit numbers, we may end up with a number we can only represent in at least $n+1$ bits
- Hardware can detect this

a and b have different signs. Will adding them ever result in overflow?

A. Yes

B. No

Adding overflow detection to add

- If a and b have different MSBs, then there is no overflow
- If a and b have the same MSB, then
 - If the output MSB is different from the input MSBs, then overflow occurred
- Another way to check for overflow: If the carry into the MSB differs from the carry out of the MSB, then overflow occurs

To check if the Carry_in is different from the Carry_out, check if

- A. $\text{Carry_in AND Carry_out} == 0$
- B. $\text{Carry_in OR Carry_out} == 1$
- C. $\text{Carry_in NOR Carry_out} == 0$
- D. $\text{Carry_in XOR Carry_out} == 1$
- E. None of the above

Reading

- Next lecture: Clocks, Latches and Flip flops
 - 3.6
- Problem set 5
 - Due Friday
- Lab 4
 - Due Monday