

CSCI 210: Computer Architecture

Lecture 16: Combinational Logic

Stephen Checkoway

Slides from Cynthia Taylor

CS History: The Traitorous Eight



From left to right: Gordon Moore, C. Sheldon Roberts, Eugene Kleiner, Robert Noyce, Victor Grinich, Julius Blank, Jean Hoerni and Jay Last. Photo by Wayne Miller.


- All worked for William Shockley, inventor of the transistor, at Shockley Semiconductor
- Shockley was paranoid and a terrible manager
- In 1957, the “Traitorous Eight” left to form Fairchild Semiconductor
- All were between 26 and 33 years old when they left
- Fairchild Semiconductor became the leader of the industry, and was involved in the creation of many other companies, including Intel and AMD

Digital Logic


- Previously: Established rules of Boolean algebra and digital logic
- Today: Building stuff!

Decoder

 - Interprets n inputs (e.g., A, B, C) as an n -bit binary number
- Sets output D_n to 1, all other outputs to 0
- The output is “one hot”




Creating a Decoder

 


- For each input signal, we need the signal and its complement
- Signals are connected to outputs via AND gates so that inputs turn on only the output that the input represents (e.g., an input value of $5 = 101_2$ turns on output D_5)

2-to-4 Decoder


2-to-4 Decoder

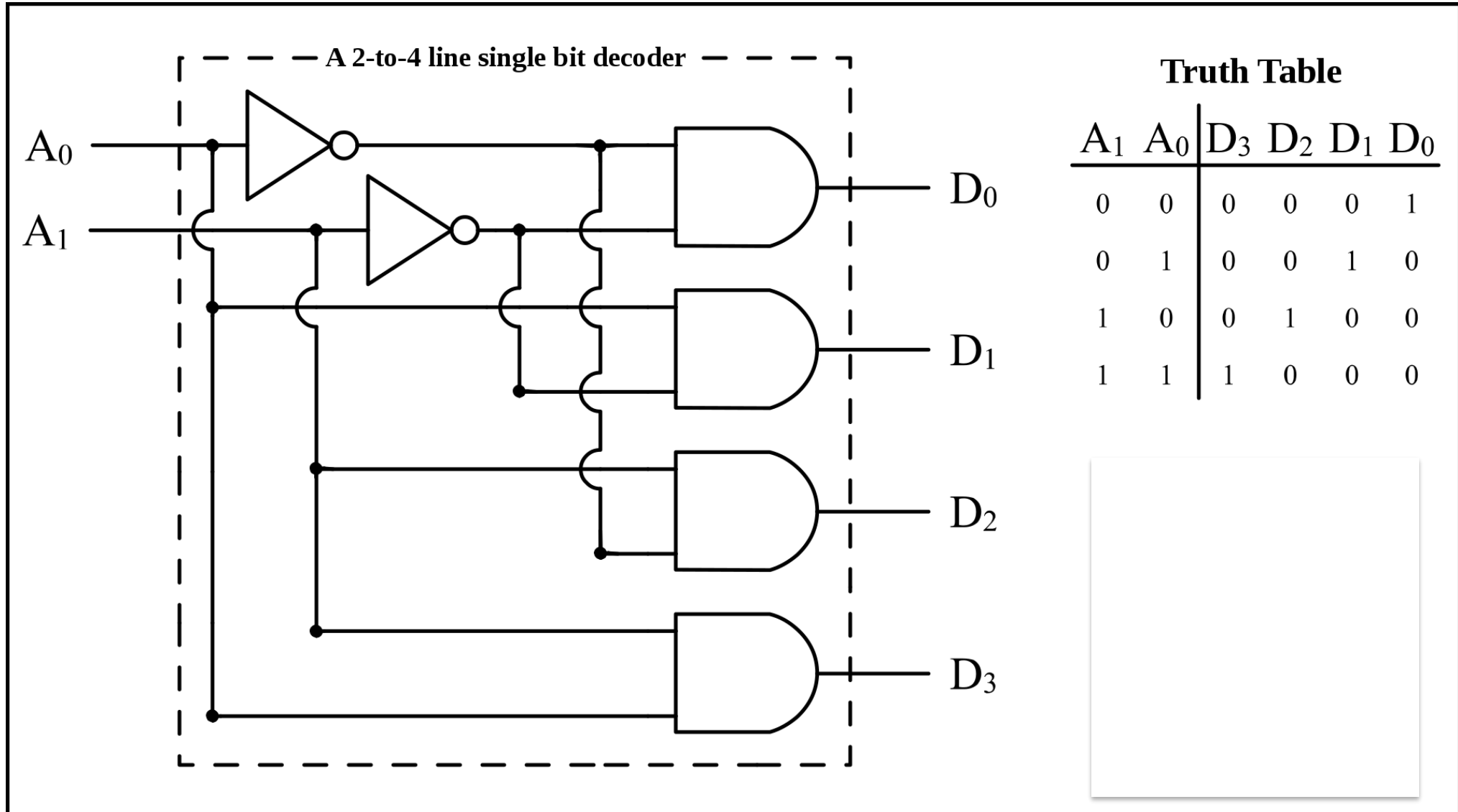


3-to-8 Decoder

 

3-to-8 Decoder, A is our MSB

 


3-to-8 Decoder, B

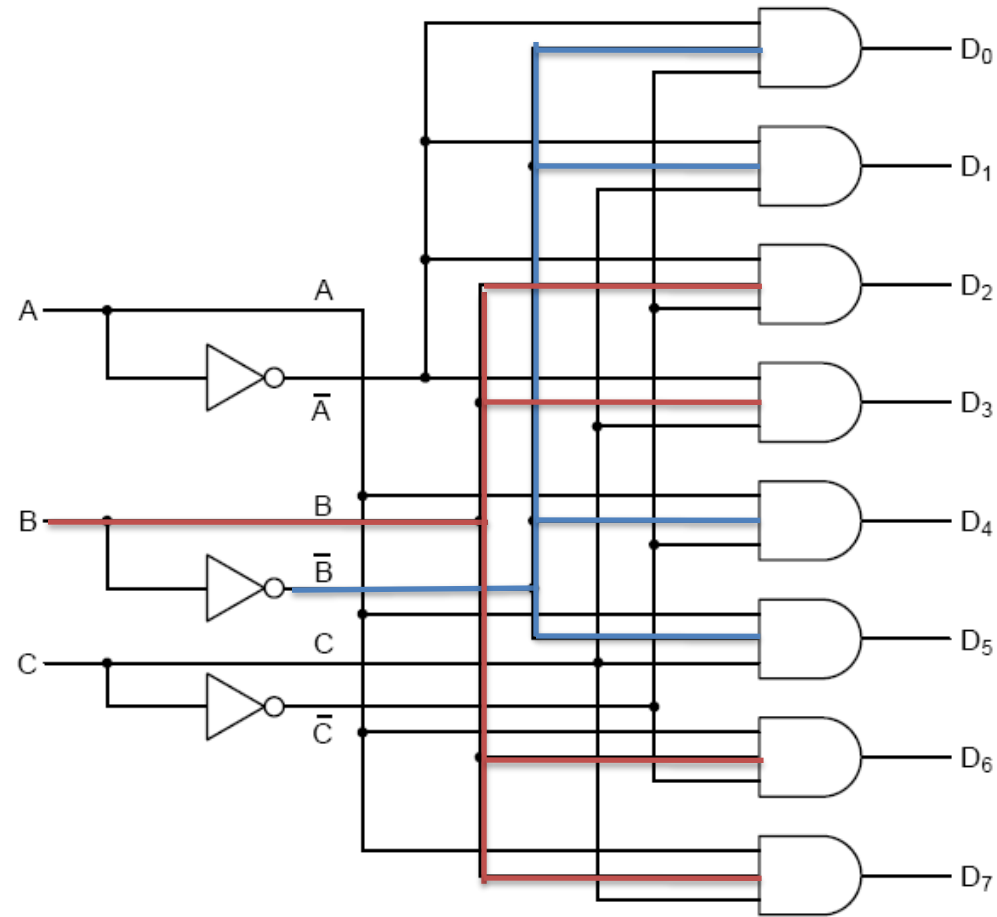


C corresponds to the lowest order bit for the input. In our 3-bit decoder, if C is 1, it sends 0 to _ and 1 to _

Clicker	0	1
A	D0, D1, D2, D3	D4, D5, D6, D7
B	D4, D5, D6, D7	D0, D1, D2, D3
C	D0, D2, D4, D6	D1, D3, D5, D7
D	D1, D3, D5, D7	D0, D2, D4, D6

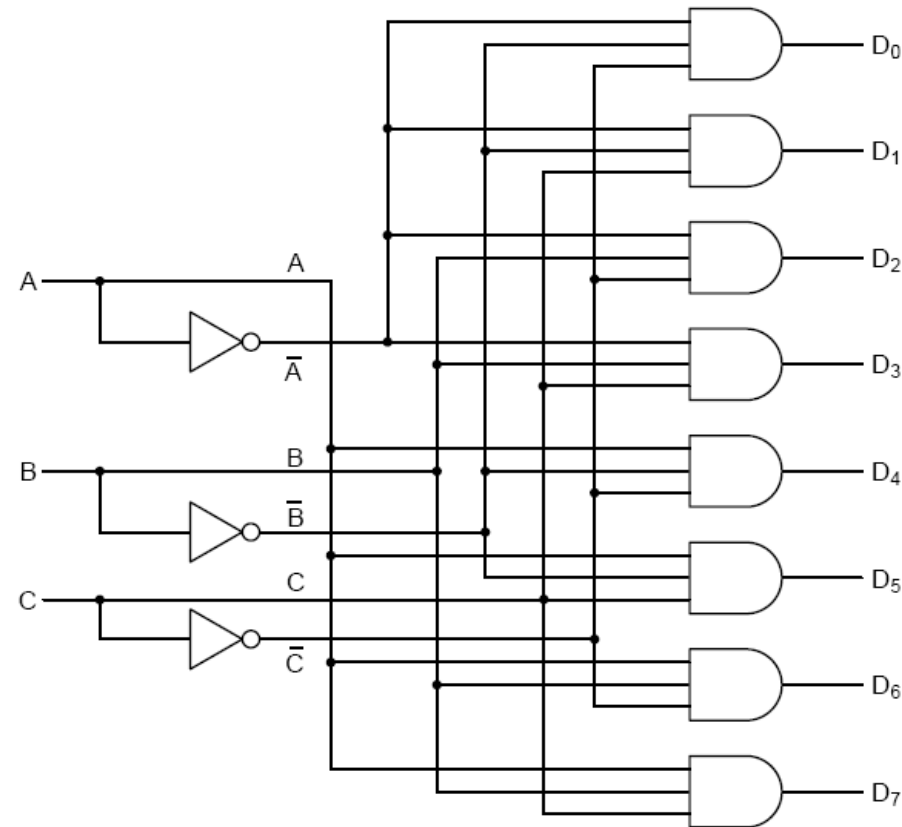


3-8 Decoder, C

 


Multiplexer

 - Select one signal from a group of 2^n inputs, to be output on a single output line.





Multiplexer

 - Lines D_0, \dots, D_7 are the data input lines and F is the output line.
- Lines A , B , and C are called the select lines. They are interpreted as a three-bit binary number, which is used to choose one of the D lines to be output on line F .




2-to-1 Multiplexer

  - S is the selector
- 0 selects A; 1 selects B
- Common circuit symbol



Implementation

A = 1, B = 0, and S is 1. C will be

 


- A. 1
- B. 0
- C. Unclear

Arbitrarily Large Multiplexer

- If there are n data inputs, there will need to be $\lceil \log_2 n \rceil$ selector inputs.
- The multiplexer consists of
 - A decoder that generates n signals, each indicating a different control value
 - An array of n AND gates, each combining one of the inputs with a signal from the decoder
 - A single large OR gate that incorporates the outputs of the AND gates


8-to-1 multiplexer

 


Scaling Up

- Have to perform combinational operations over an entire word (32-bits) of input.
- Bus: a collection of data lines that is treated together as a single logical signal.
- Example: A multiplexer is used to choose which of the two buses (each 32 bits wide) will be written into the Result register

Replicating a 1-bit Multiplexer 32 times

 

a. A 32-bit wide 2-to-1 multiplexer

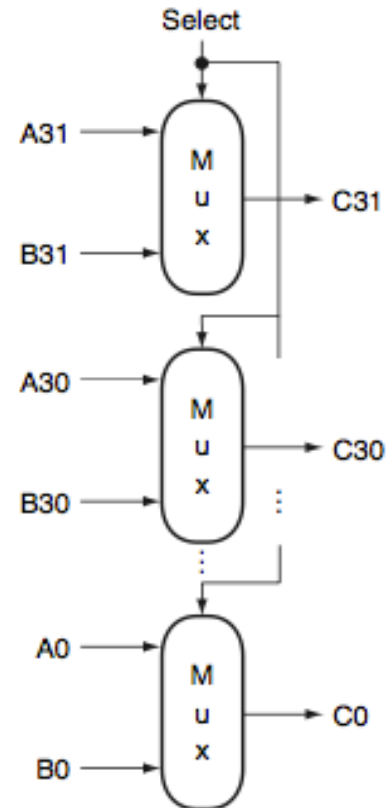


b. The 32-bit wide multiplexer is actually an array of 32 1-bit multiplexers


Will the Select value be the same for each mux?

A. Yes

B. No

 

a. A 32-bit wide 2-to-1 multiplexor

 

b. The 32-bit wide multiplexor is actually an array of 32 1-bit multiplexors