CSCI 210: Computer Architecture
Lecture 29: More Pipelining

Stephen Checkoway
Oberlin College
May 4, 2022
Slides from Cynthia Taylor

Announcements

- Problem Set 9 due Friday
- Lab 8 due Sunday
- Office hours today 13:30–14:30

MIPS Pipeline

Five stages, one step per stage, one clock cycle per stage

1. IF: Instruction fetch from memory
2. ID: Instruction decode & register read
3. EX: Execute operation or calculate address
4. MEM: Access memory operand
5. WB: Write result back to register

Execution in a Pipelined Datapath

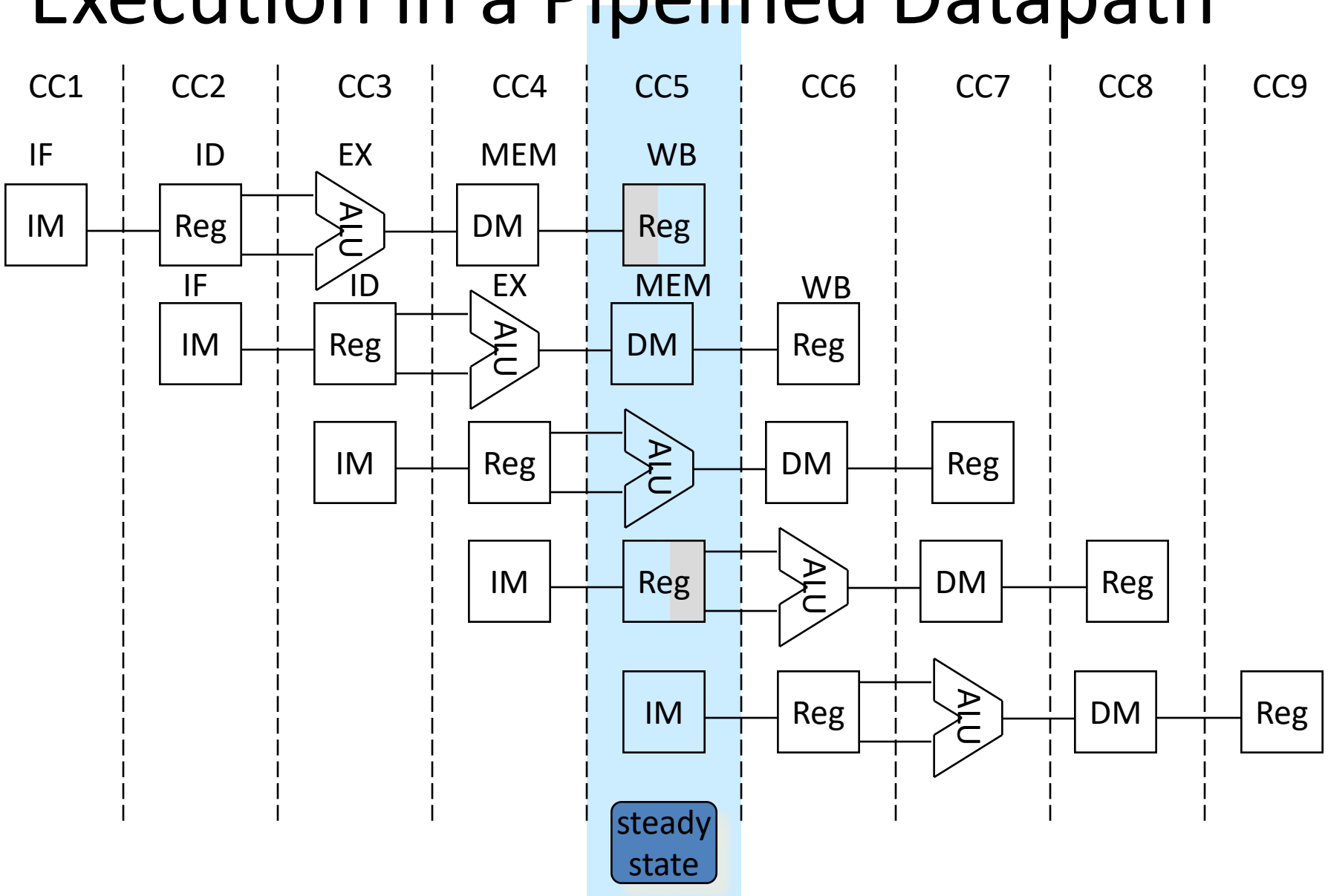

Single Cycle Datapath

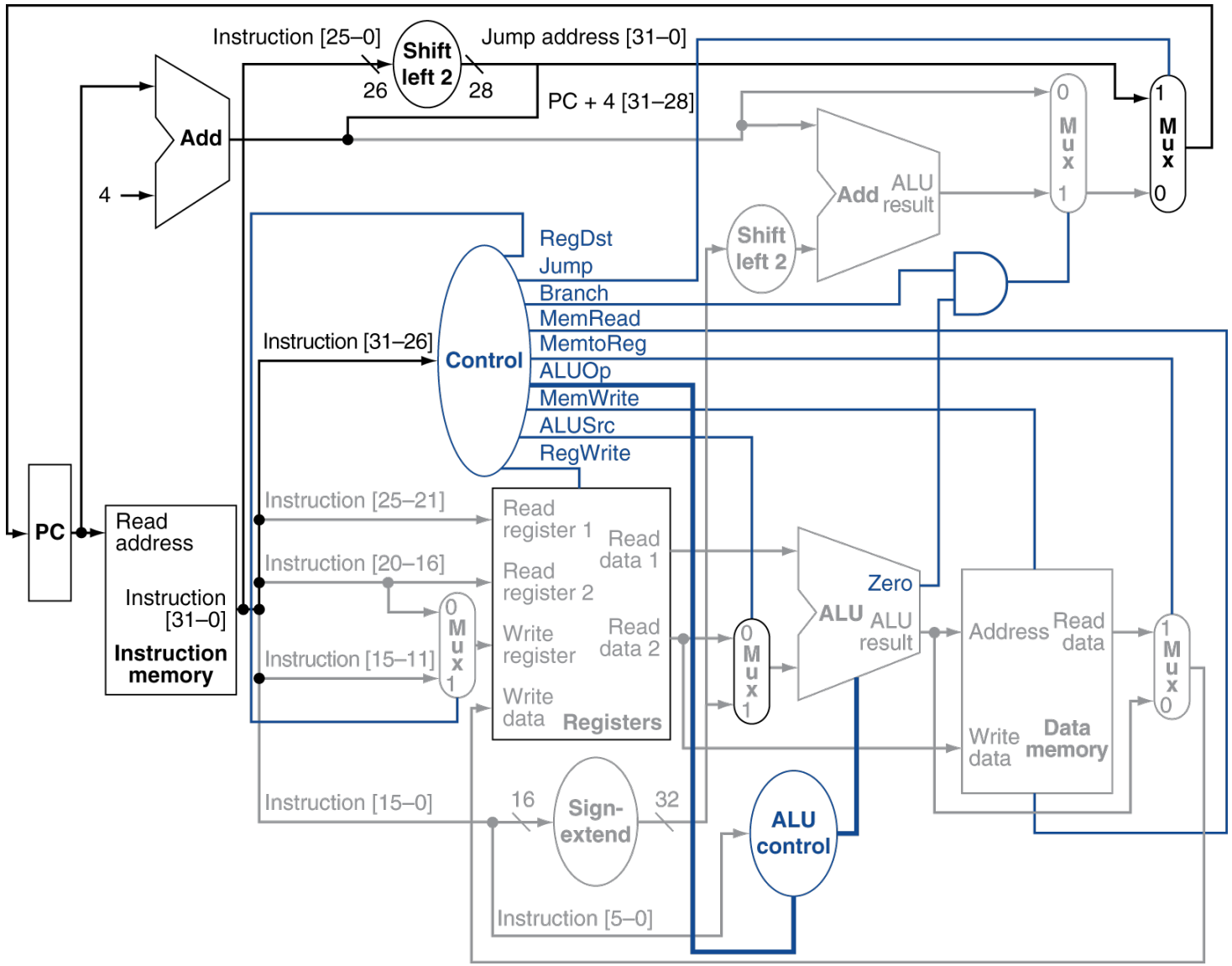

Pipeline registers

- Need registers between stages
  - To hold information produced in previous cycle

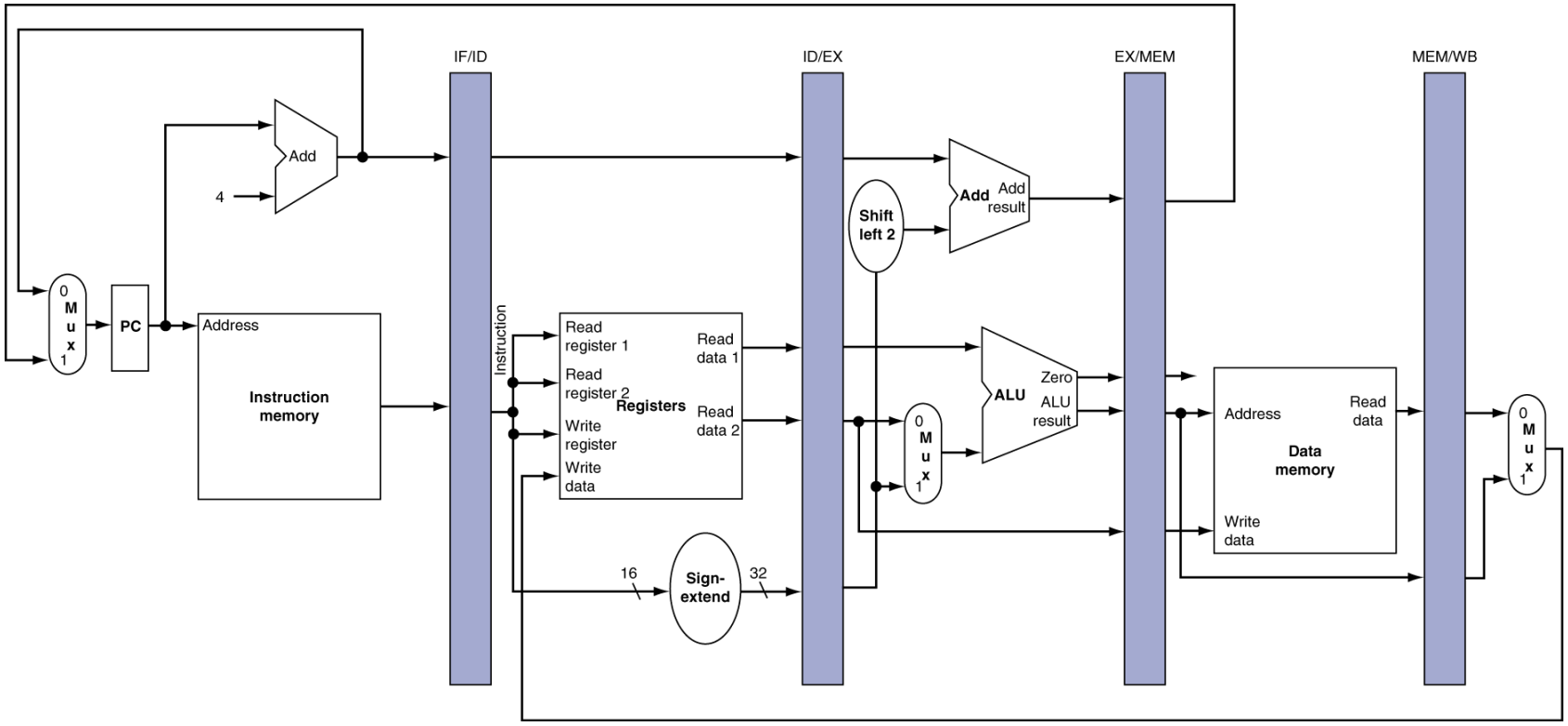

IF for Load, Store, …

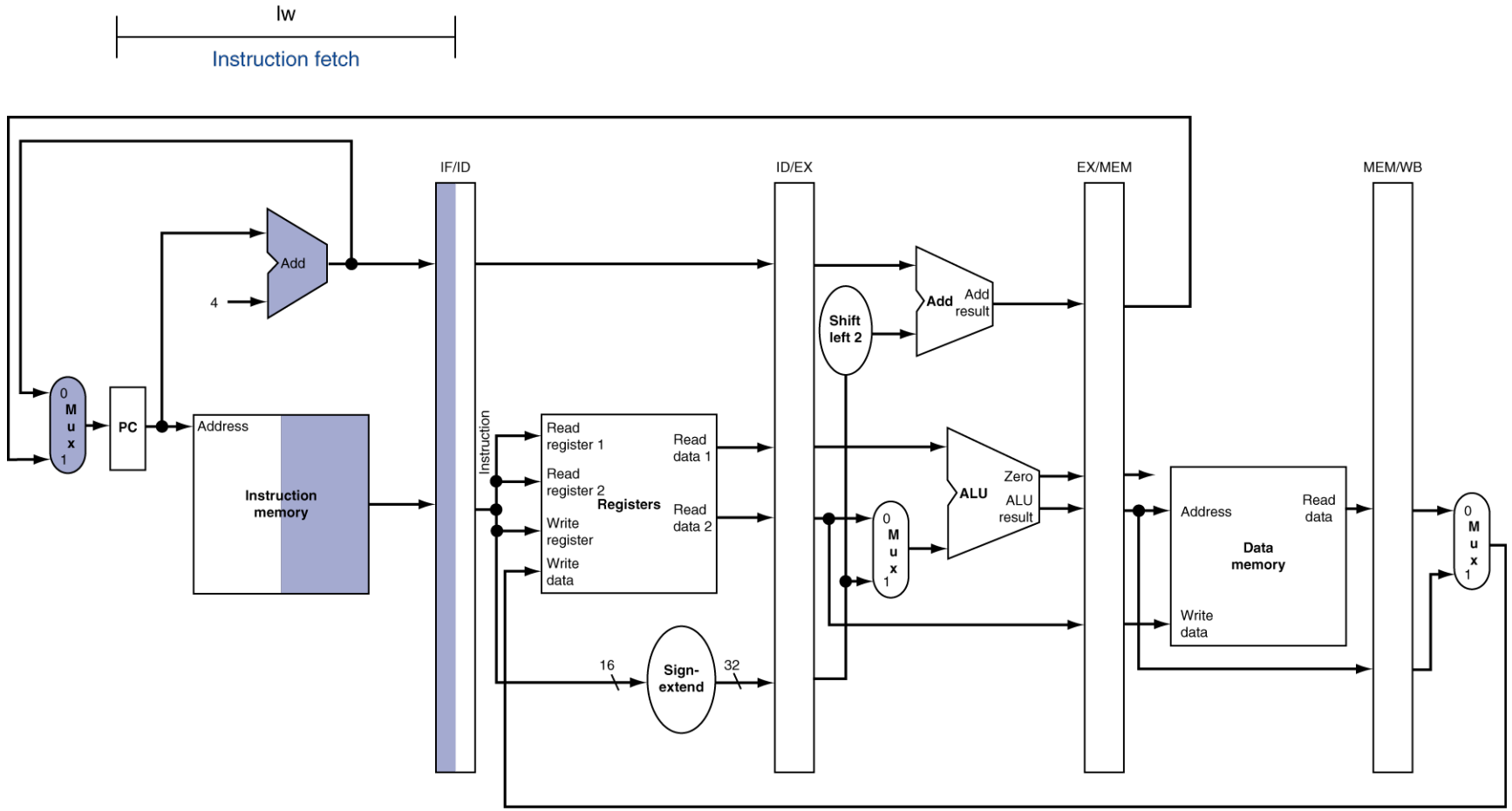

ID for Load, Store, …

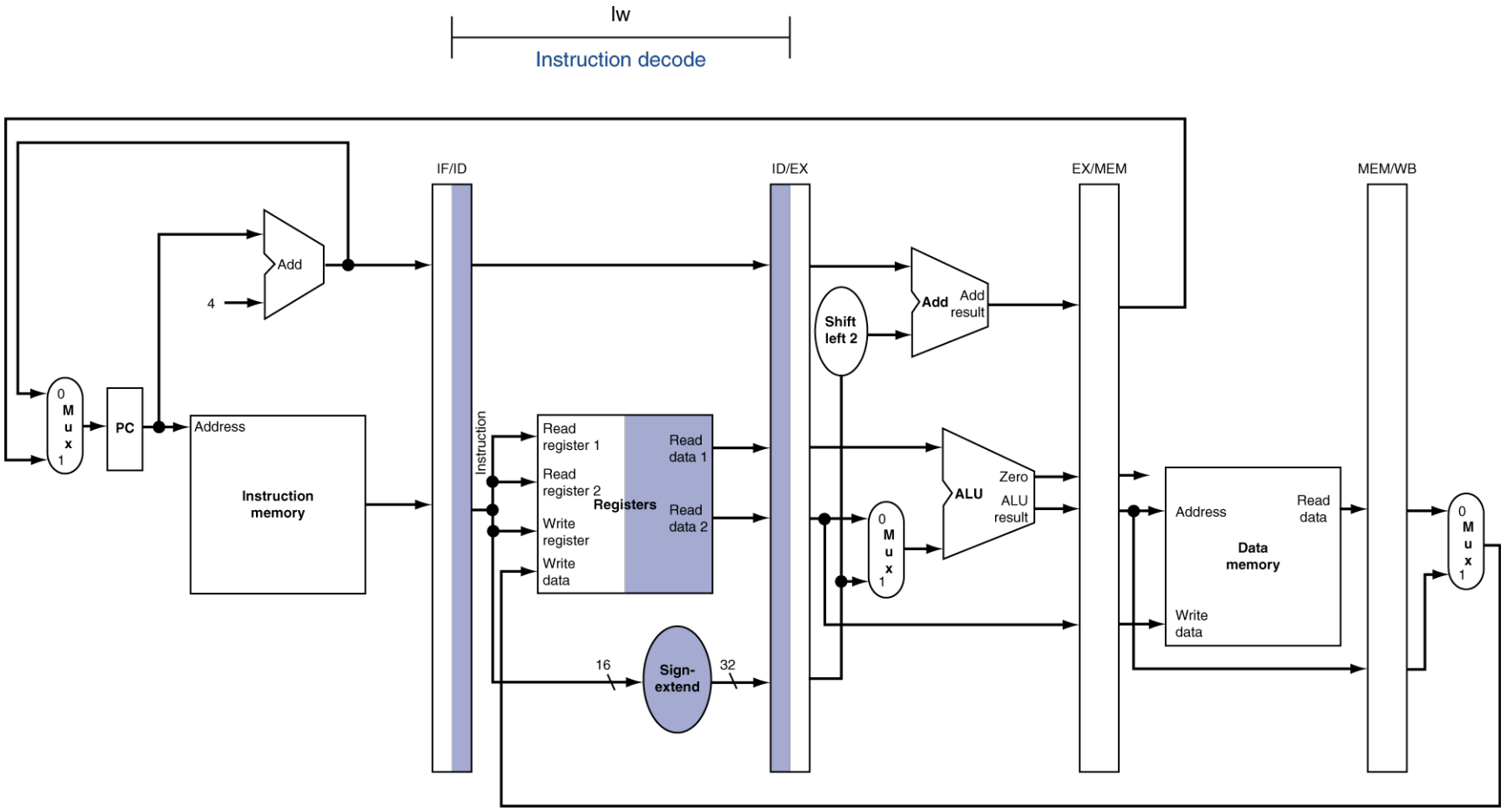

The register file will output data from both read registers, but load will only use one of them. We should

A. Save both of them in ID/EX

B. Only save the one we will use in ID/EX

C. Do something else

EX for Load

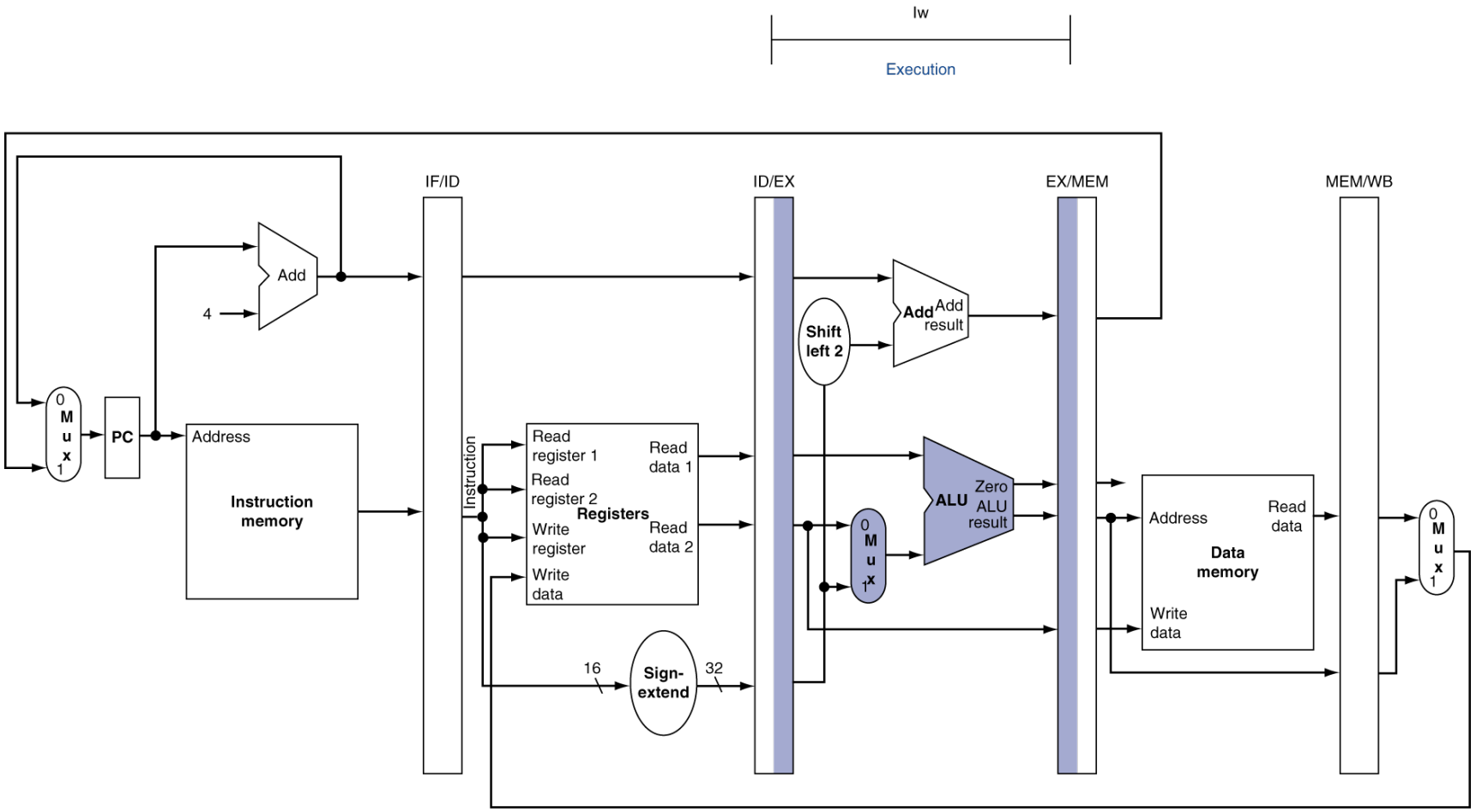
lw
Execution
IF/ID
ID/EX
EX/MEM
MEM/WB
Add
4
0
M
u
x
1
PC
Address
Instruction memory
Instruction
Read register 1
Read register 2
Registers
Write register
Write data
Read data 1
Read data 2
16
Sign-extend
32
Shift left 2
Add
Add result
ALU
Zero
ALU result
Address
Read data
Data memory
Write data

MEM for Load

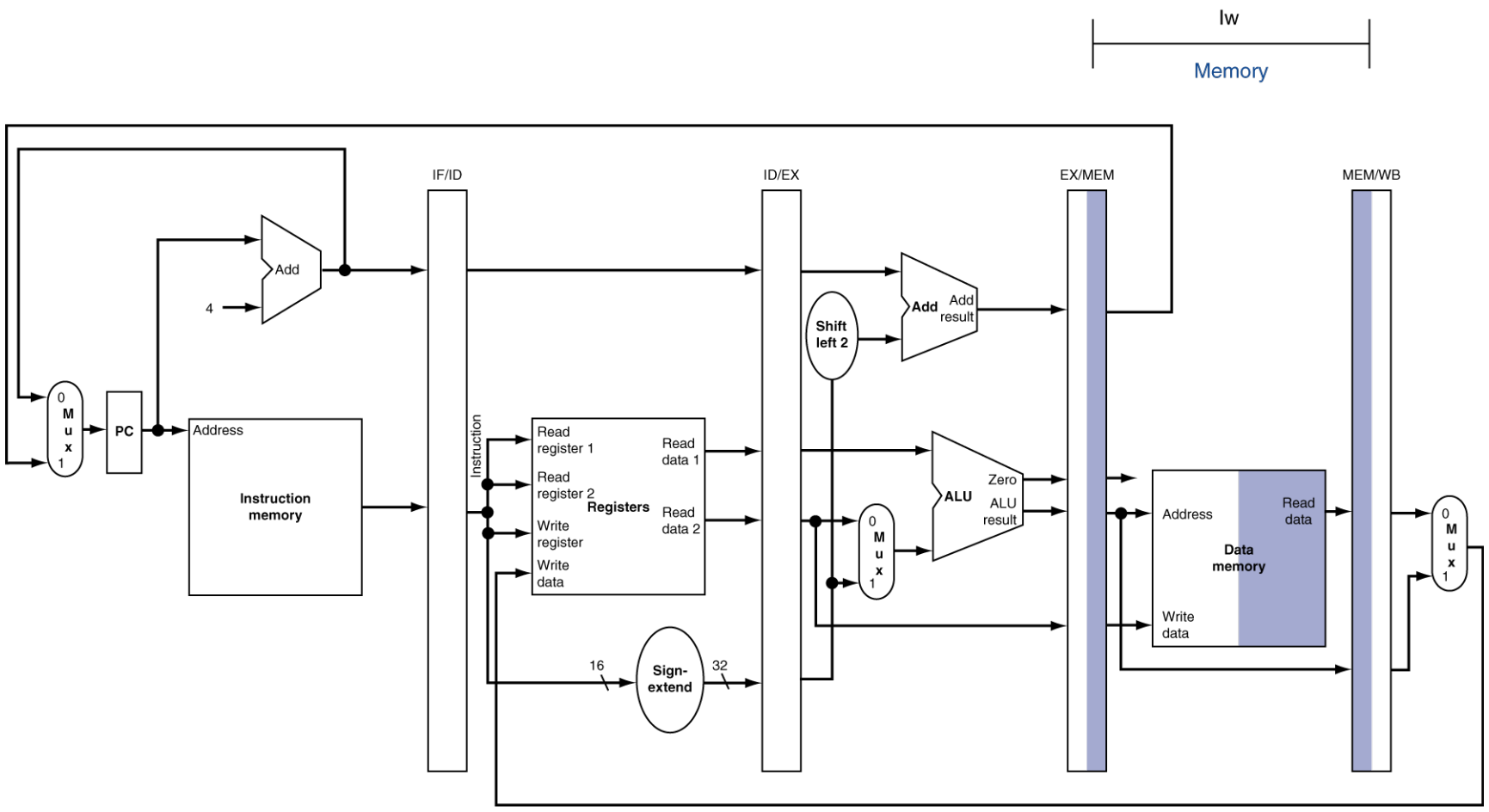
lw
Memory
IF/ID
ID/EX
EX/MEM
MEM/WB
Add
4
0
M
u
x
1
PC
Address
Instruction memory
Instruction
Read register 1
Read register 2
Registers
Write register
Write data
Read data 1
Read data 2
16
Sign-extend
32
Shift left 2
Add
Add result
ALU
Zero
ALU result
Address
Data memory
Read data
Write data

When we do WB for load

A. Everything will be fine

B. The data to write to the register will be wrong

C. The register number to write to will be wrong

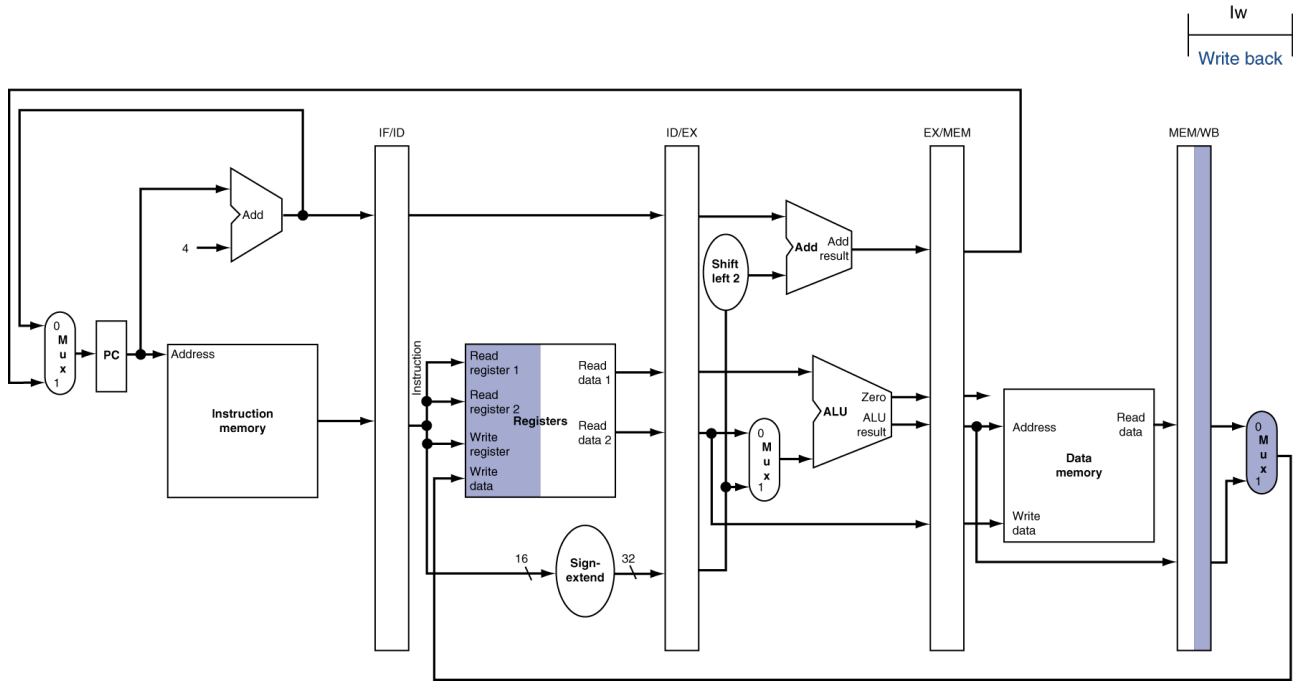

WB for Load

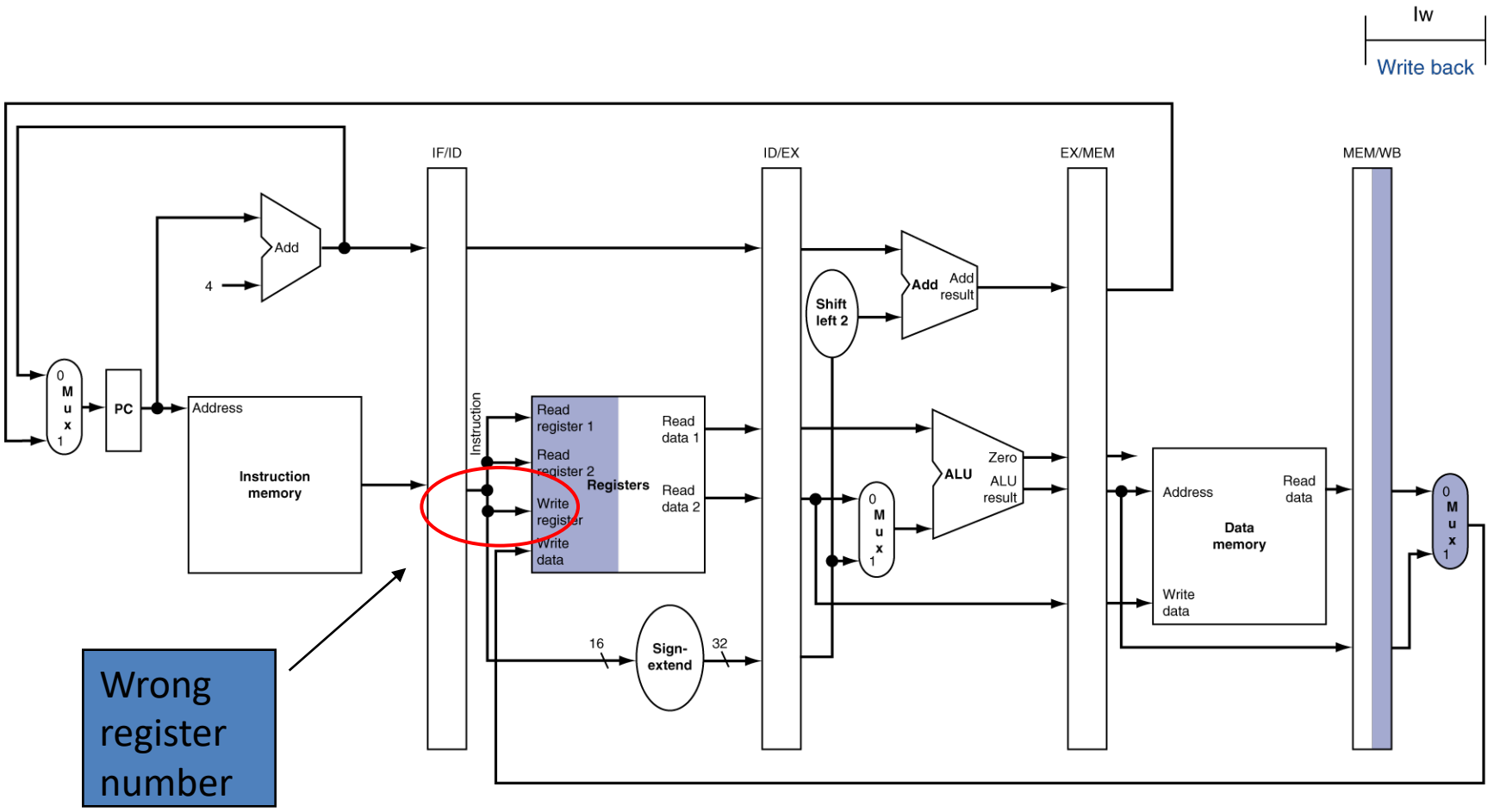
lw
Write back
IF/ID
ID/EX
EX/MEM
MEM/WB
Add
4
M u x
0
1
PC
Address
Instruction memory
Instruction
Read register 1
Read register 2
Registers
Write register
Write data
Read data 1
Read data 2
16
Sign-extend
32
Shift left 2
Add
Add result
ALU
Zero
ALU result
Address
Read data
Data memory
Write data
Wrong register number

Corrected Datapath for Load

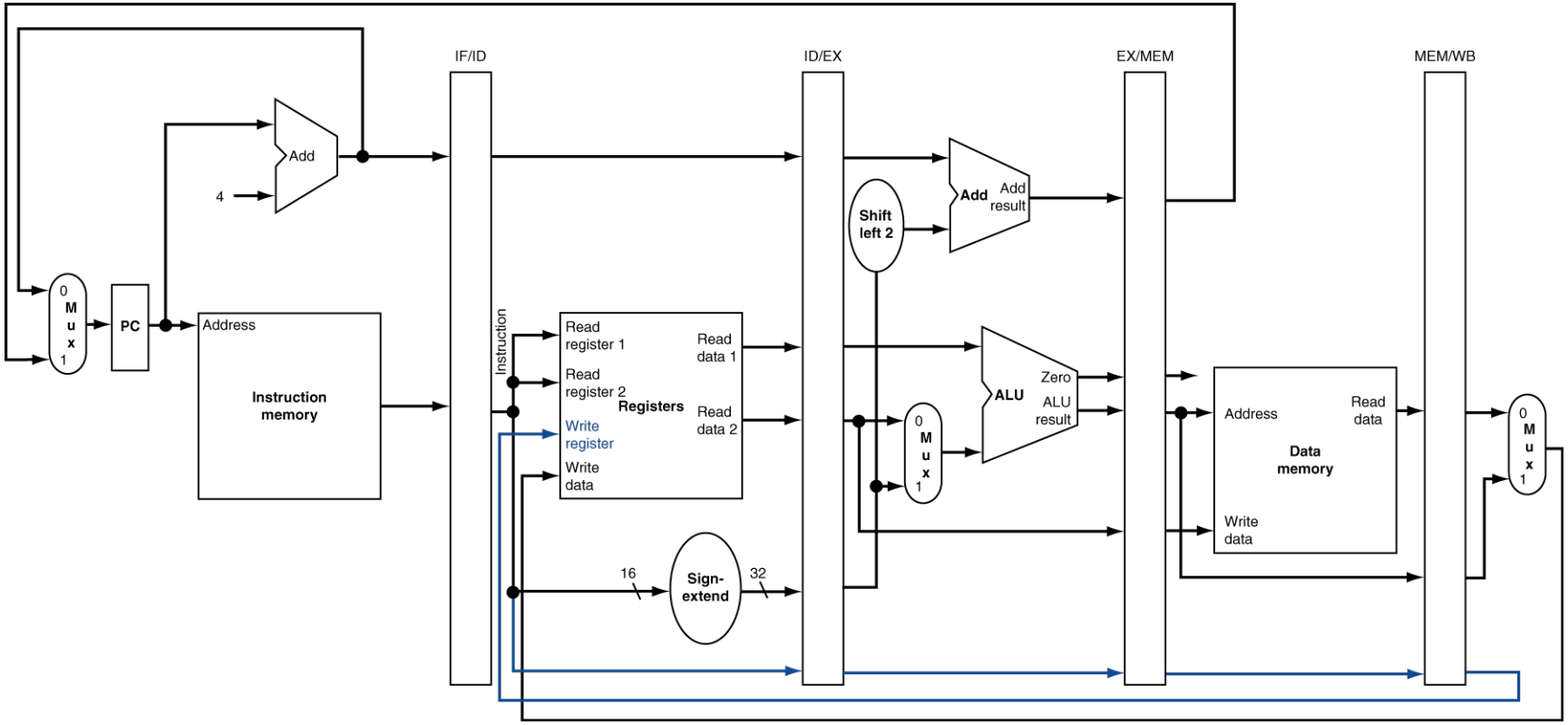

EX for Store

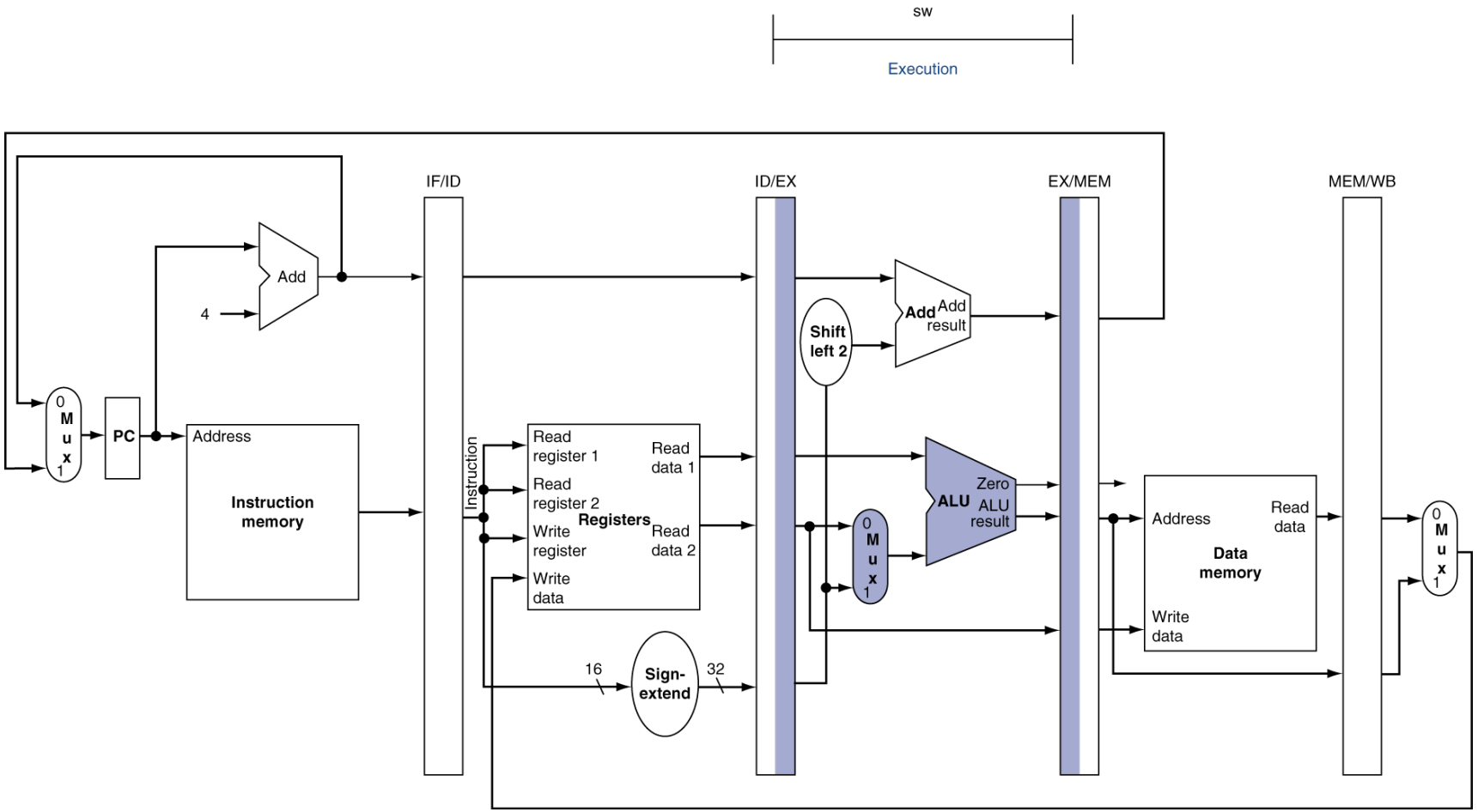
sw
Execution
IF/ID
ID/EX
EX/MEM
MEM/WB
Add
4
M
u
x
0
1
PC
Address
Instruction memory
Instruction
Read register 1
Read register 2
Registers
Write register
Write data
Read data 1
Read data 2
16
Sign-extend
32
Shift left 2
Add
Add result
ALU
Zero
ALU result
Address
Read data
Data memory
Write data

MEM for Store

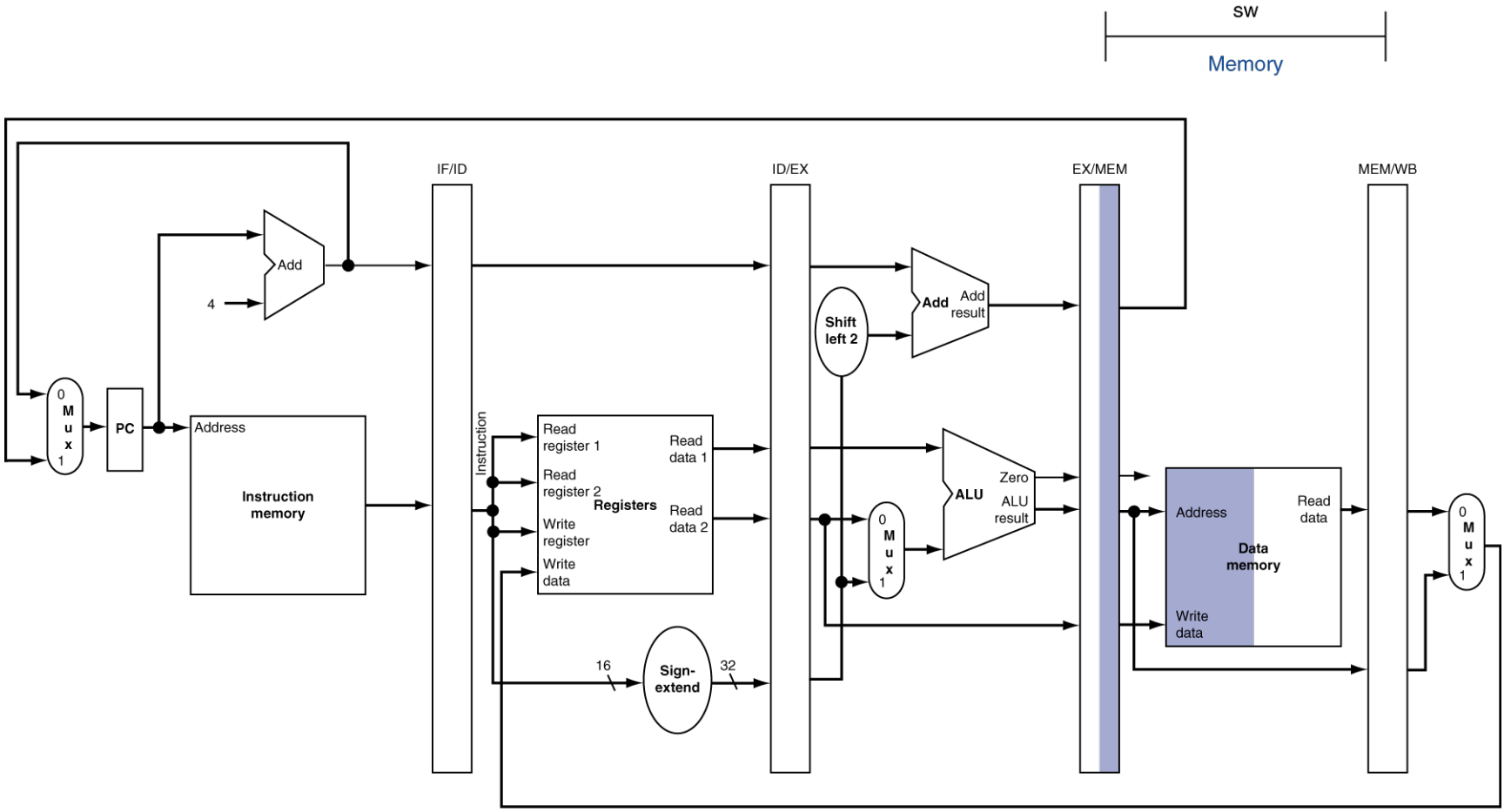

WB for Store

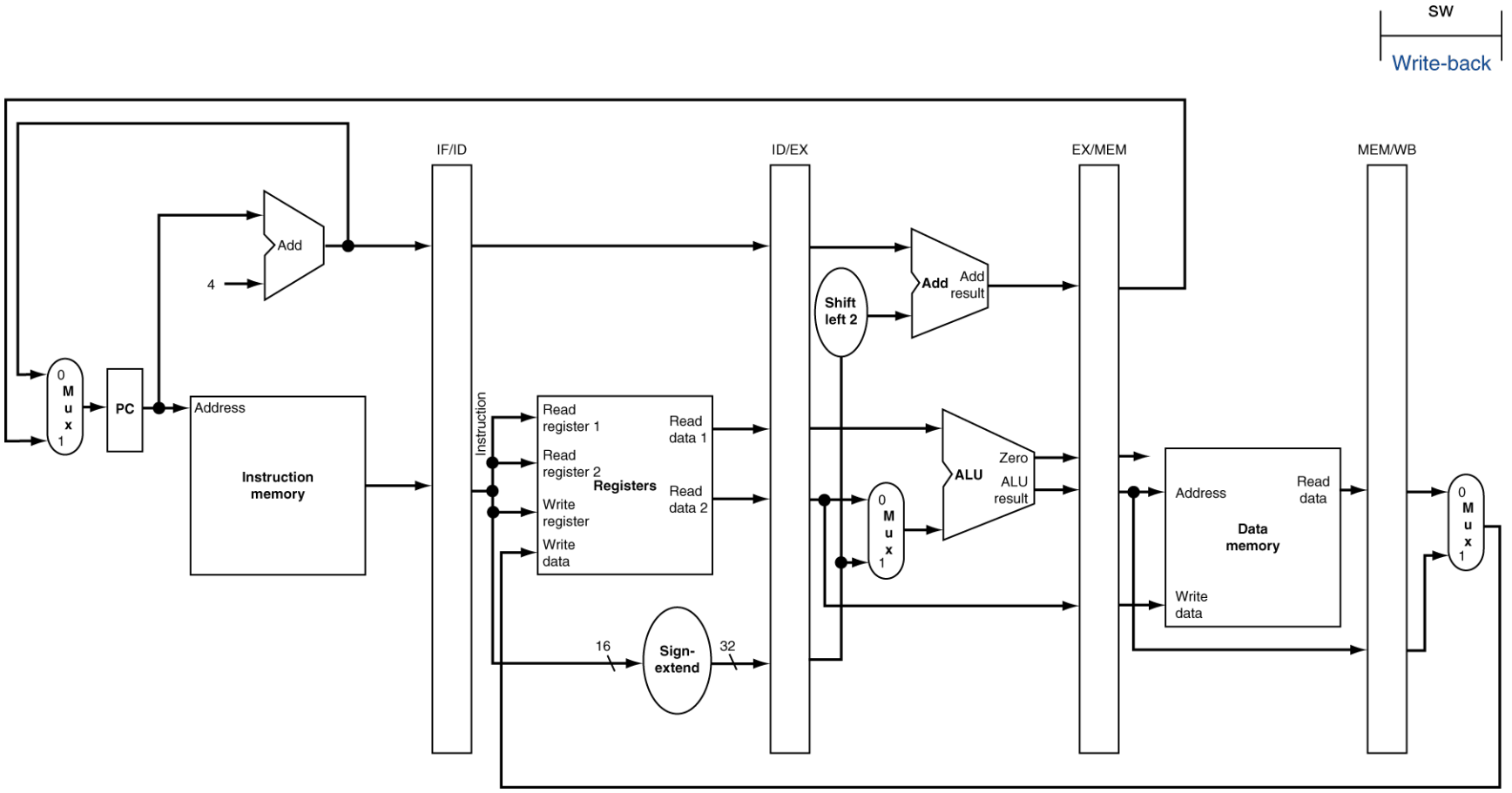
SW
Write-back
IF/ID
ID/EX
EX/MEM
MEM/WB
Add
4
0
M
u
x
1
PC
Address
Instruction memory
Instruction
Read register 1
Read register 2
Registers
Write register
Write data
Read data 1
Read data 2
16
Sign-extend
32
Shift left 2
Add
Add result
ALU
Zero
ALU result
Address
Read data
Data memory
Write data

Reading

- Next lecture: Pipelined Datapath
  - Section 5.7

- Problem Set 9 due Friday

- Lab 8 due Sunday